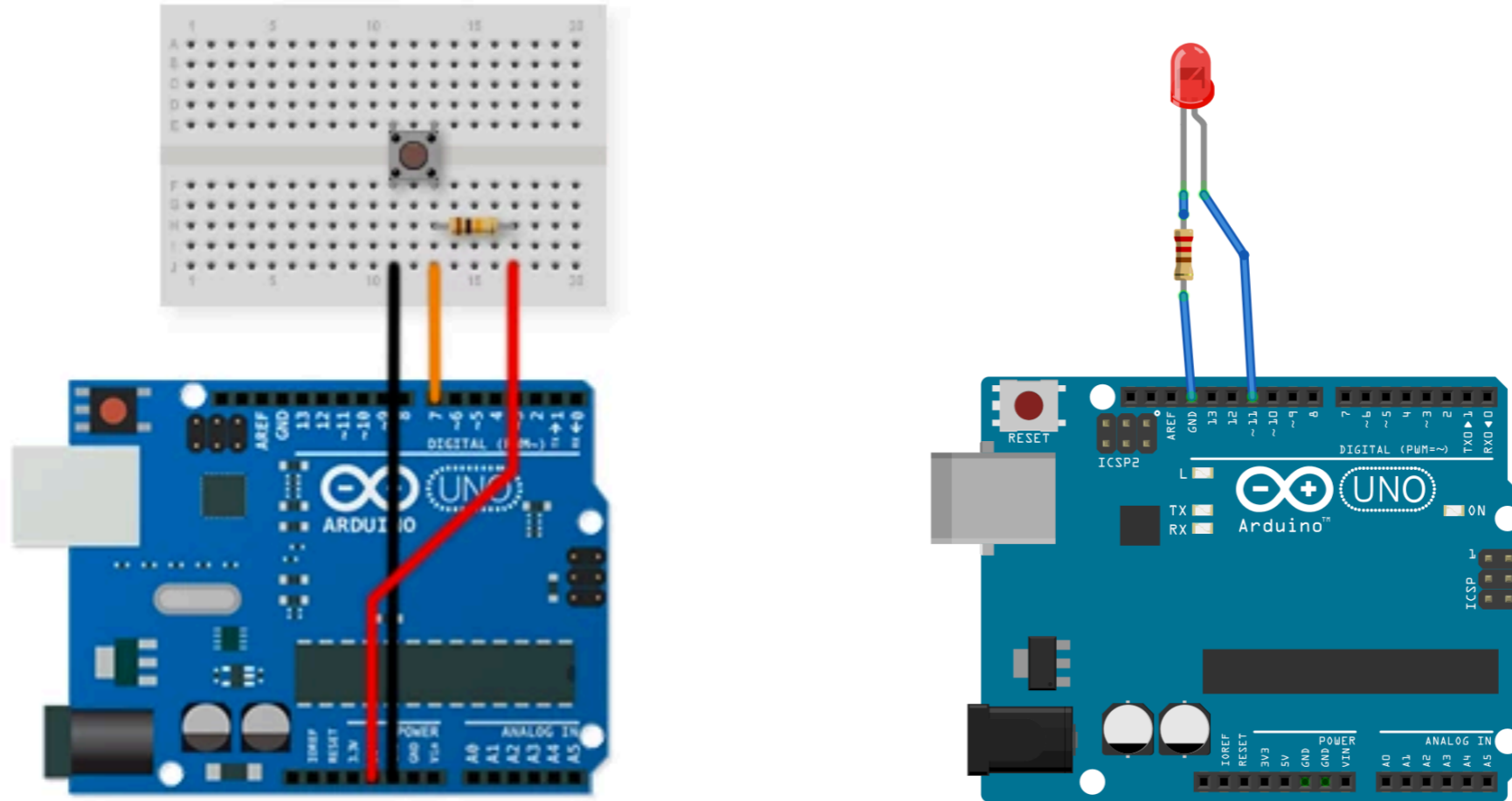



Physical Computing 2021




## Exercise 2.3: Digital Input

Combine the two circuits to  
create an led you can turn on  
with your switch

**Pull Up**

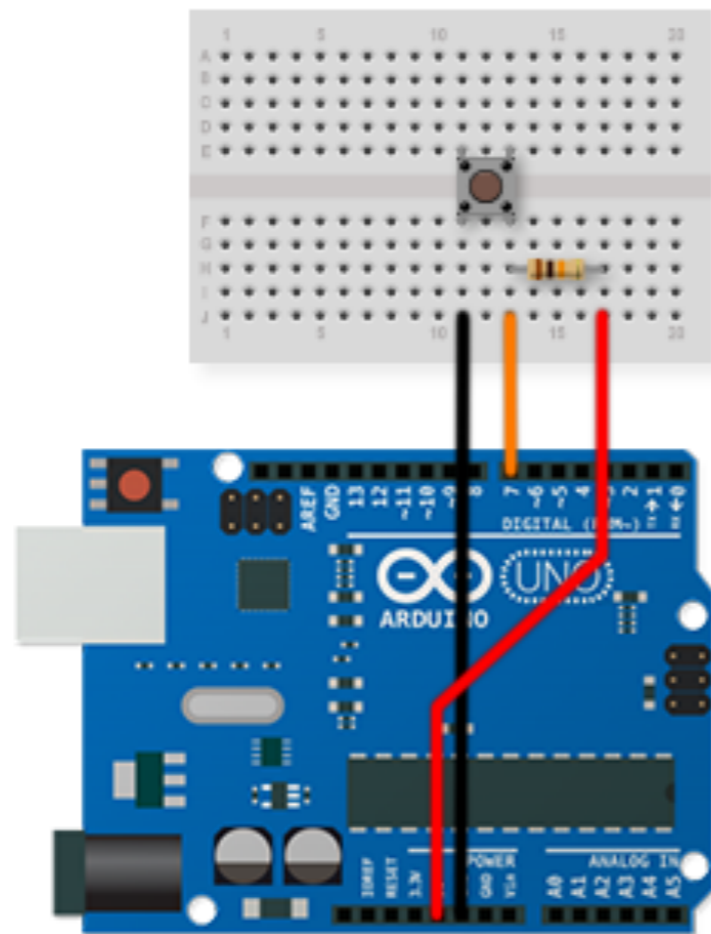

**Pull Down**

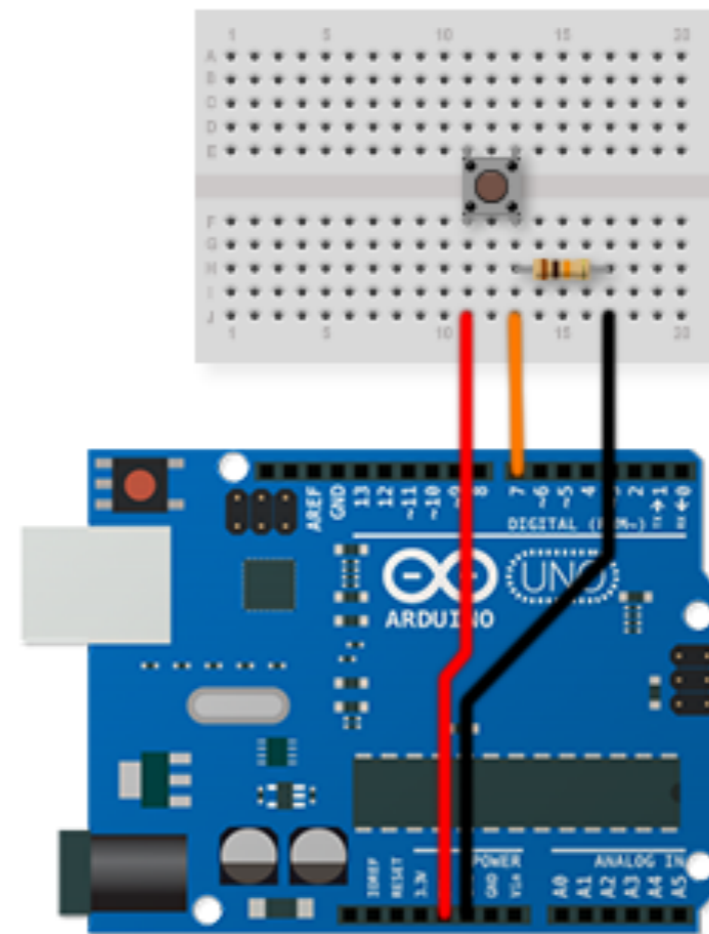

**Internal Pull Up**


```
pinMode(5, INPUT_PULLUP)
```

**Digital Inputs**
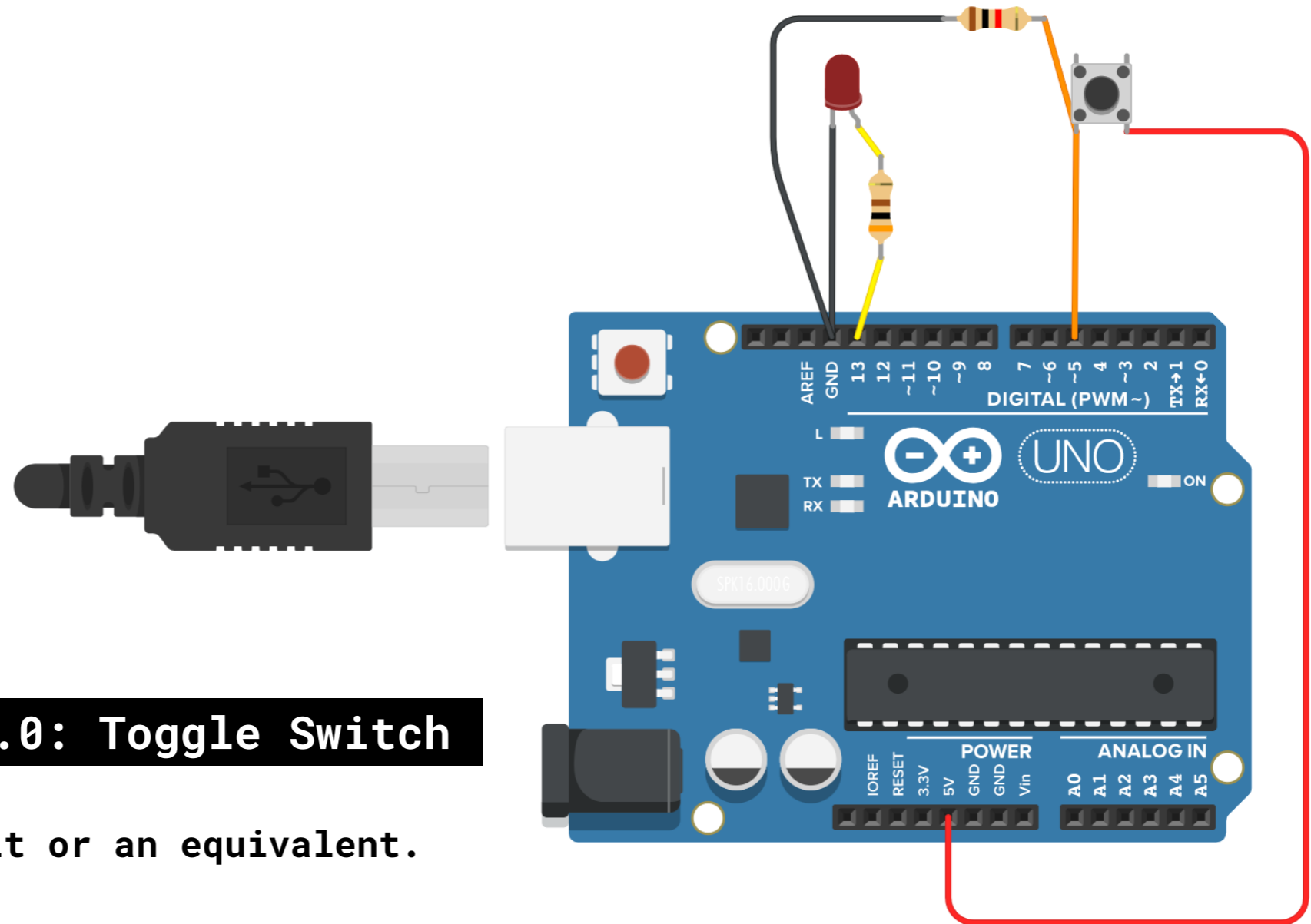
## Exercise PC1.0: Toggle Switch

Build this circuit or an equivalent.


Code it so that the LED stays on after one press, and then turns off after the next press i.e a toggle switch.




The multimeter is an essential tool for problem solving in electronics!




## The Multimeter

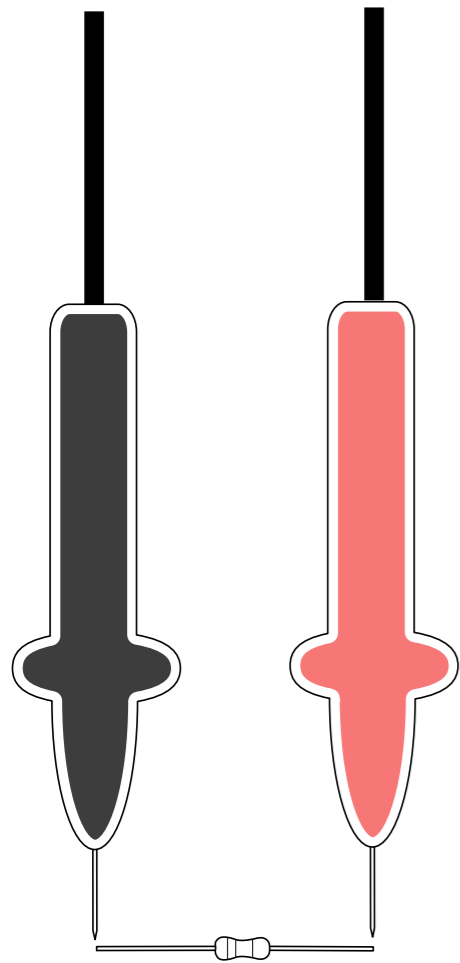

Resistance

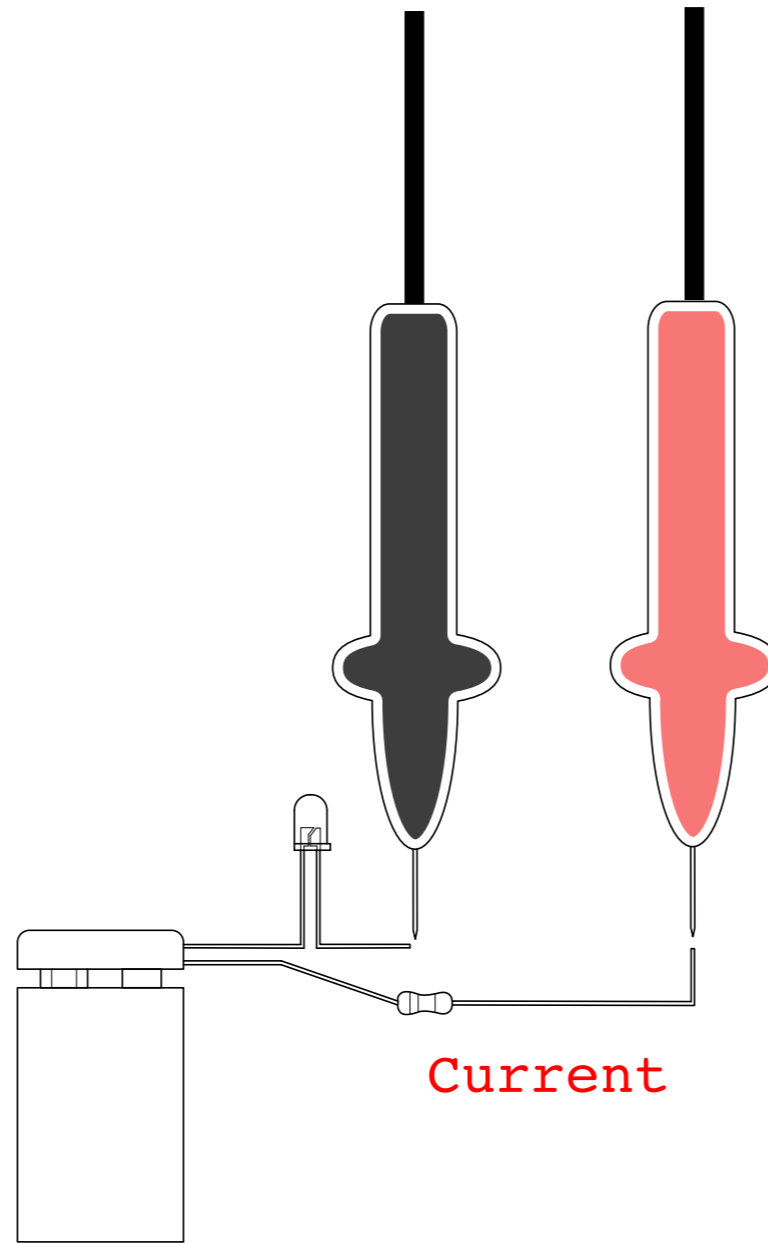


Current

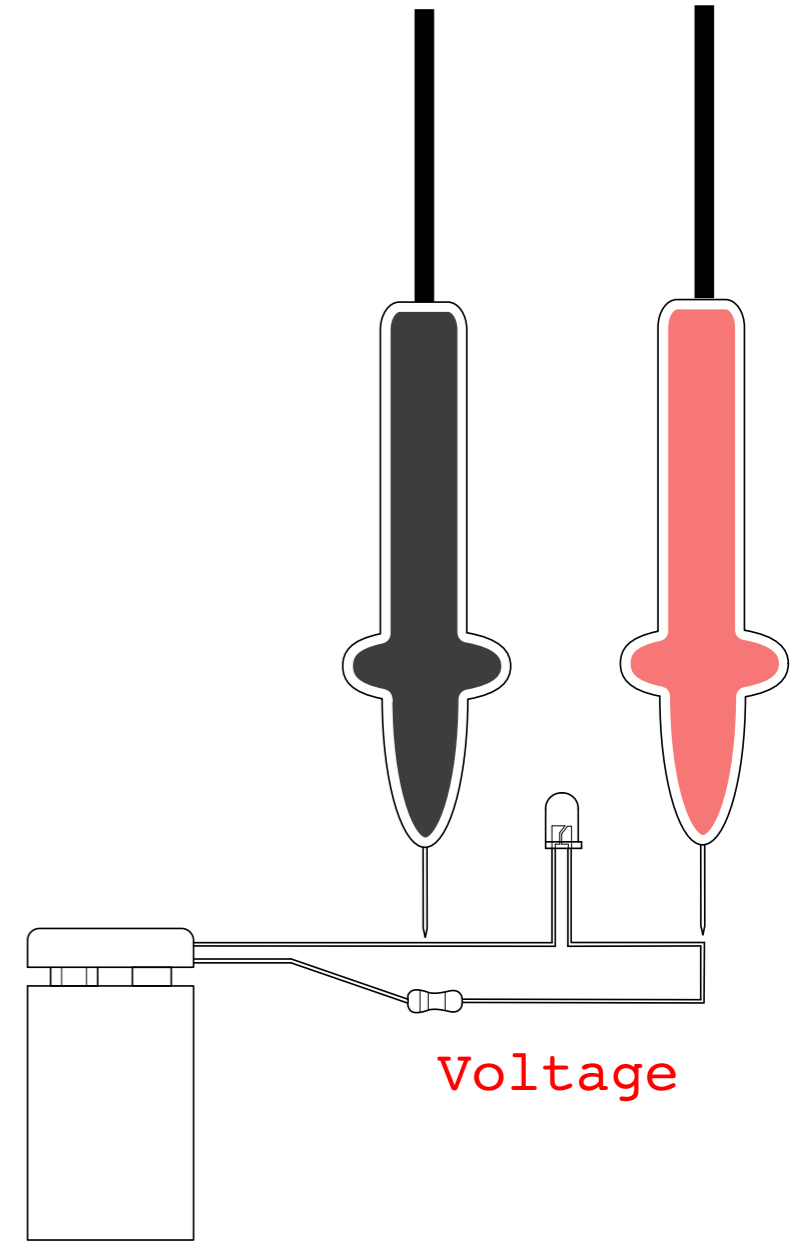

Voltage



The way we use the probes on a multimeter depends on what we are testing! Resistance of components should (ideally) be tested outside its circuit. For current we have to break the circuit, and insert the probes to close it again. Voltage, however, can be measure between any two points.

## The Multimeter

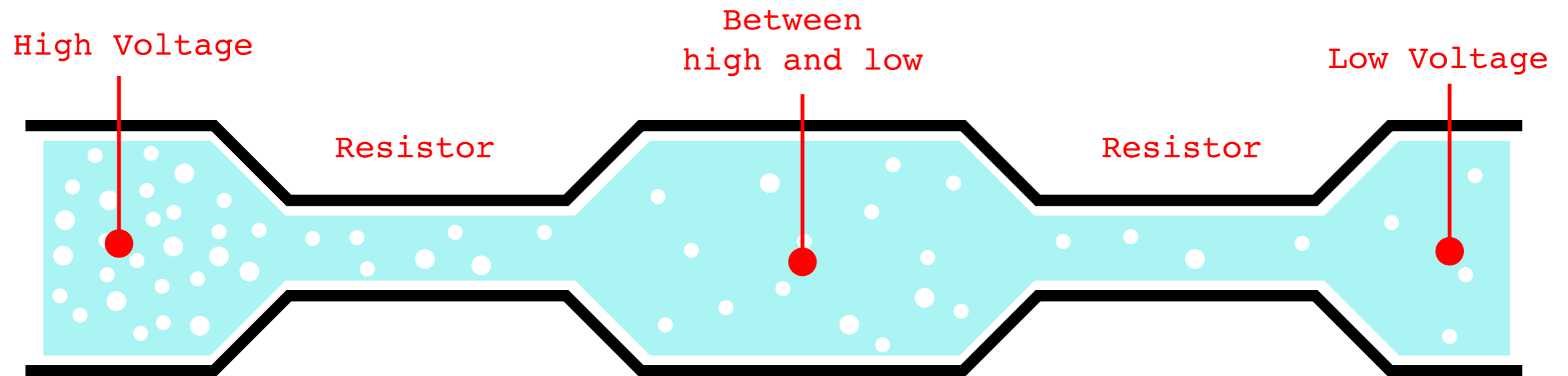

Voltage will drop when current flow through any component that converts electricity to some other form of energy.

## Voltage Divider

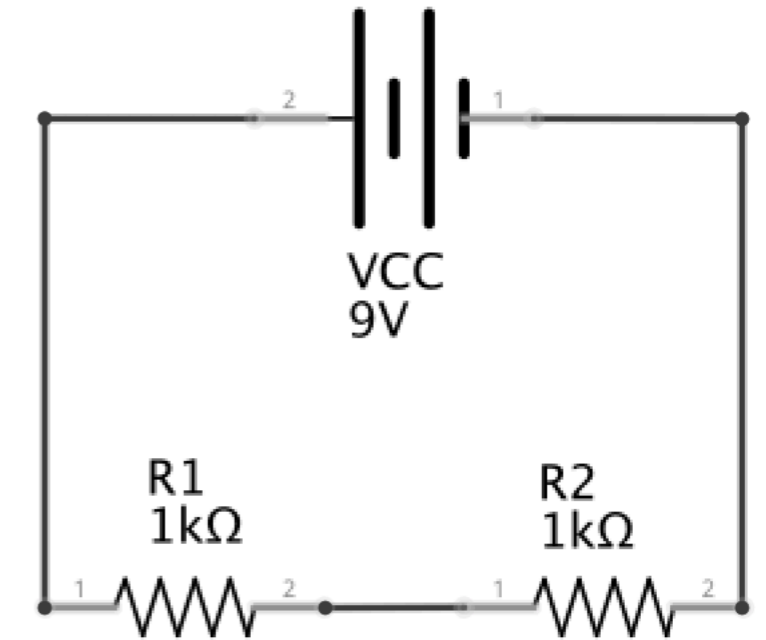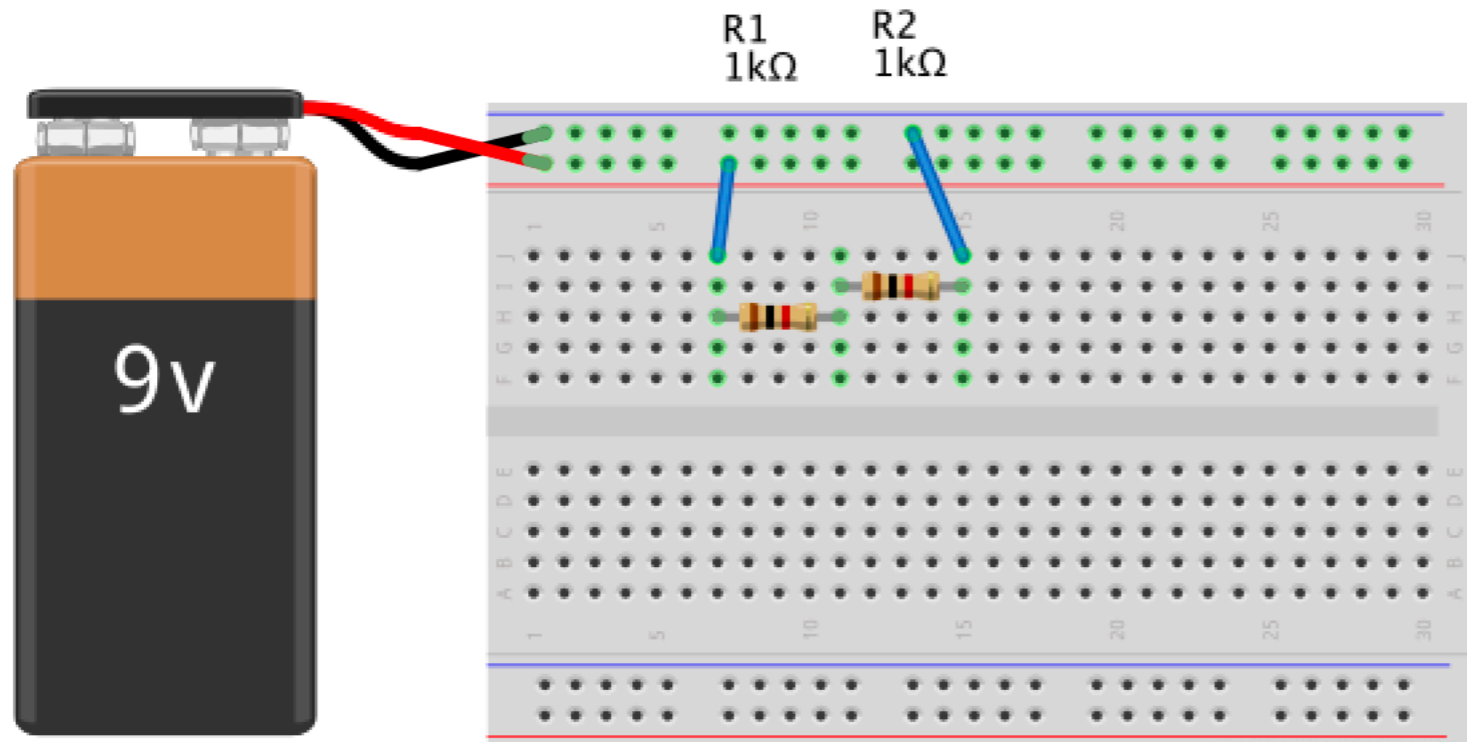


## Exercise PC1.1: Voltage Divider

Assembly the circuit with resistors of two different values. Try calculating the voltage between your resistors, and check with the multimeter if it's correct.


$$V_{res} = V_{cc} \times \frac{R_2}{(R_1 + R_2)}$$

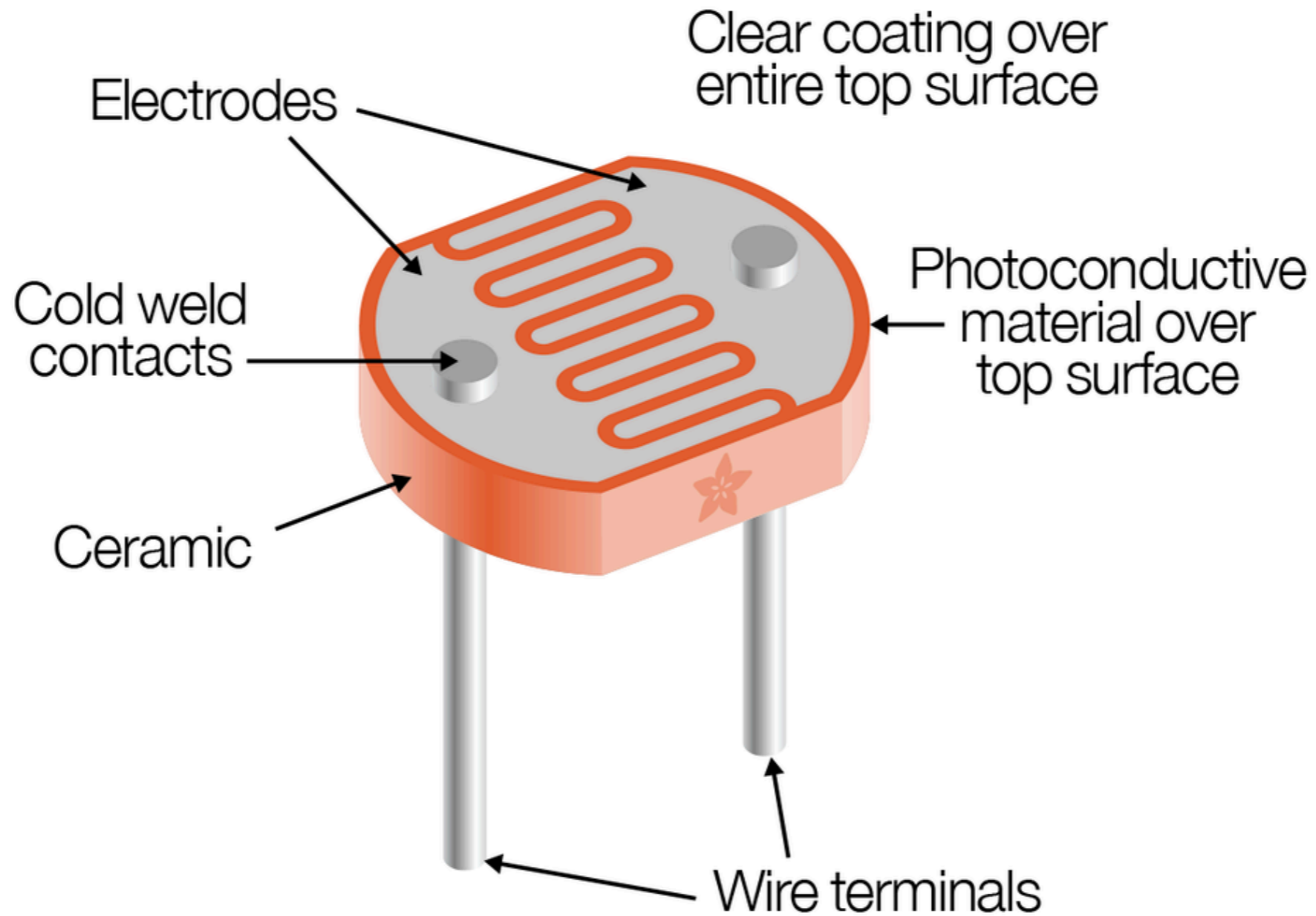$V_{res}$  = resulting voltage  
 $V_{cc}$  = applied voltage (9V)  
 $R_1$  = first resistor (1000 ohm)  
 $R_2$  = second resistor (1000 ohm)








**Analog Sensors**

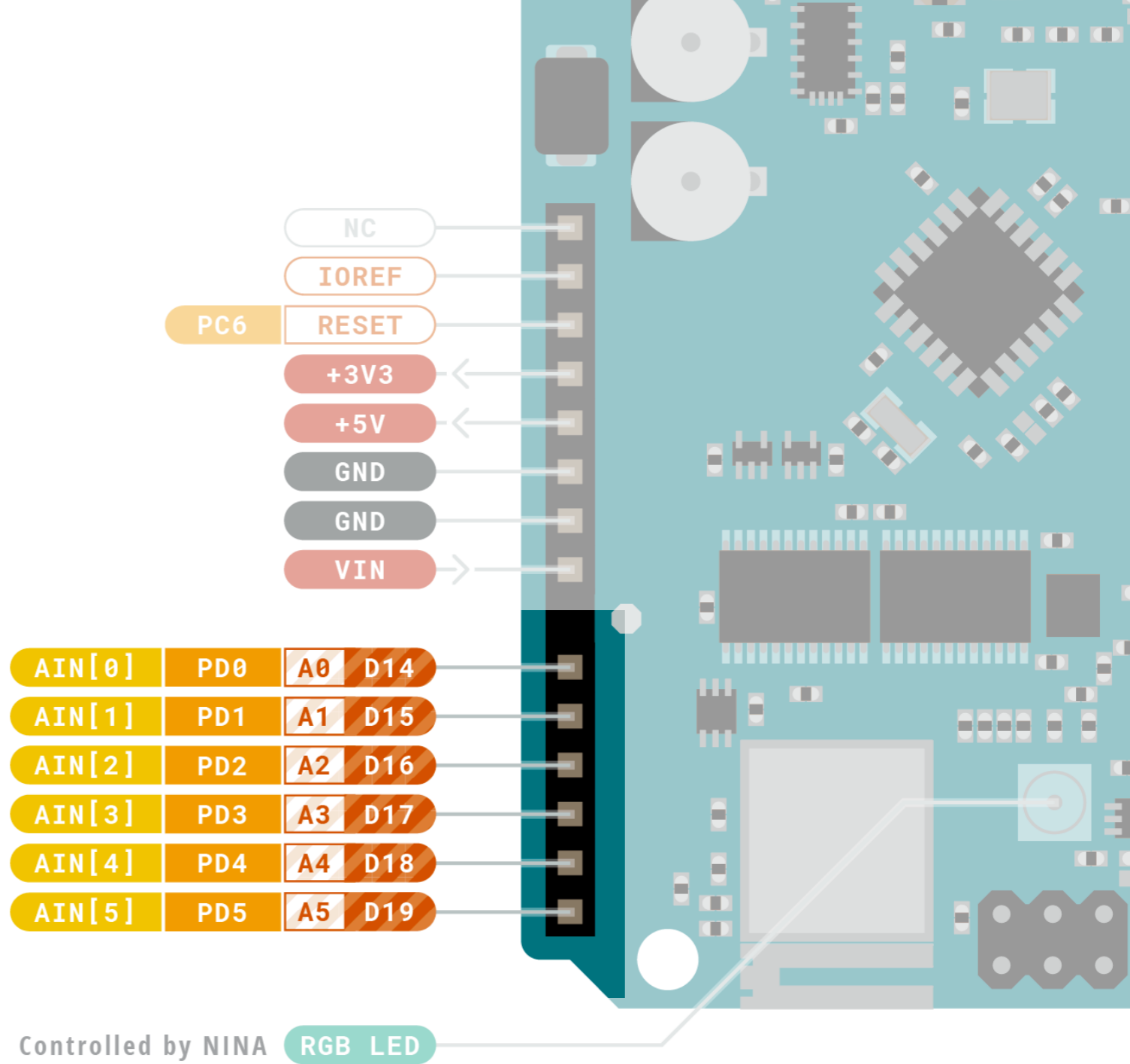

## Analog Pins

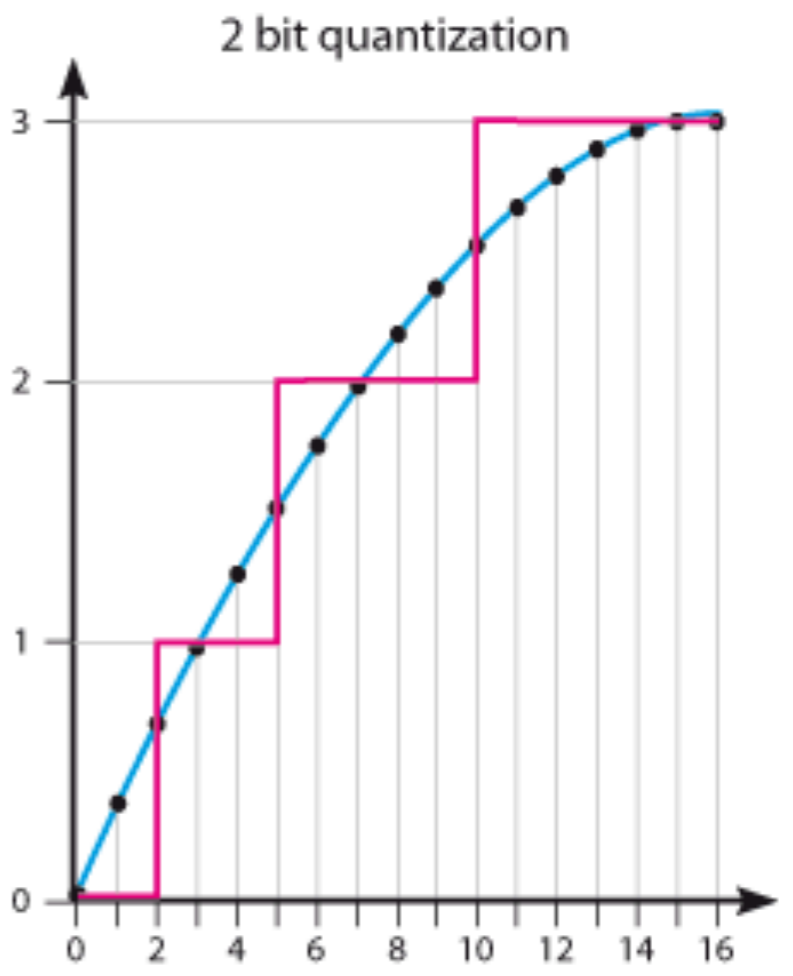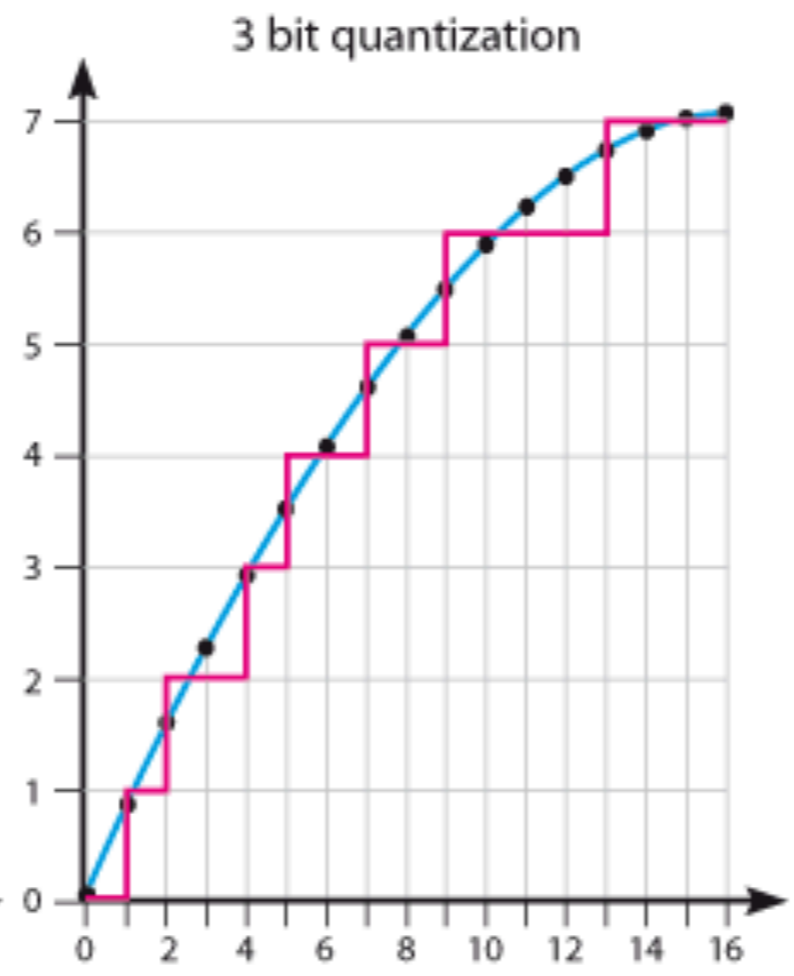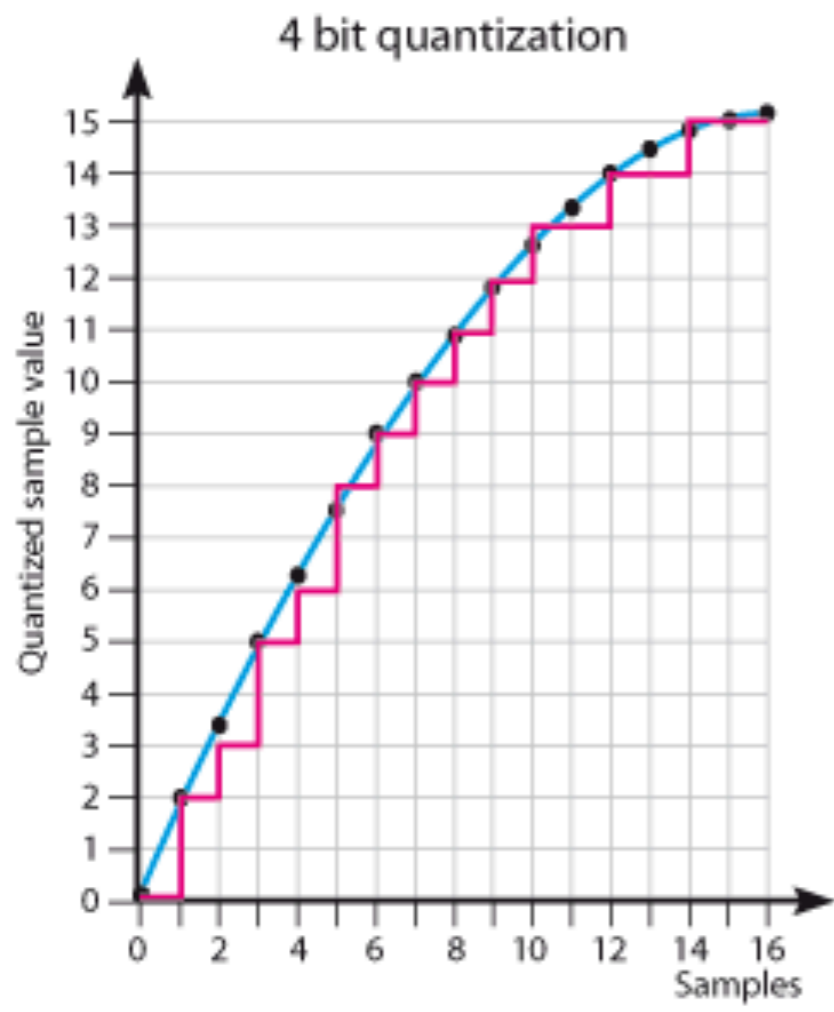


**Analog to Digital Conversion**

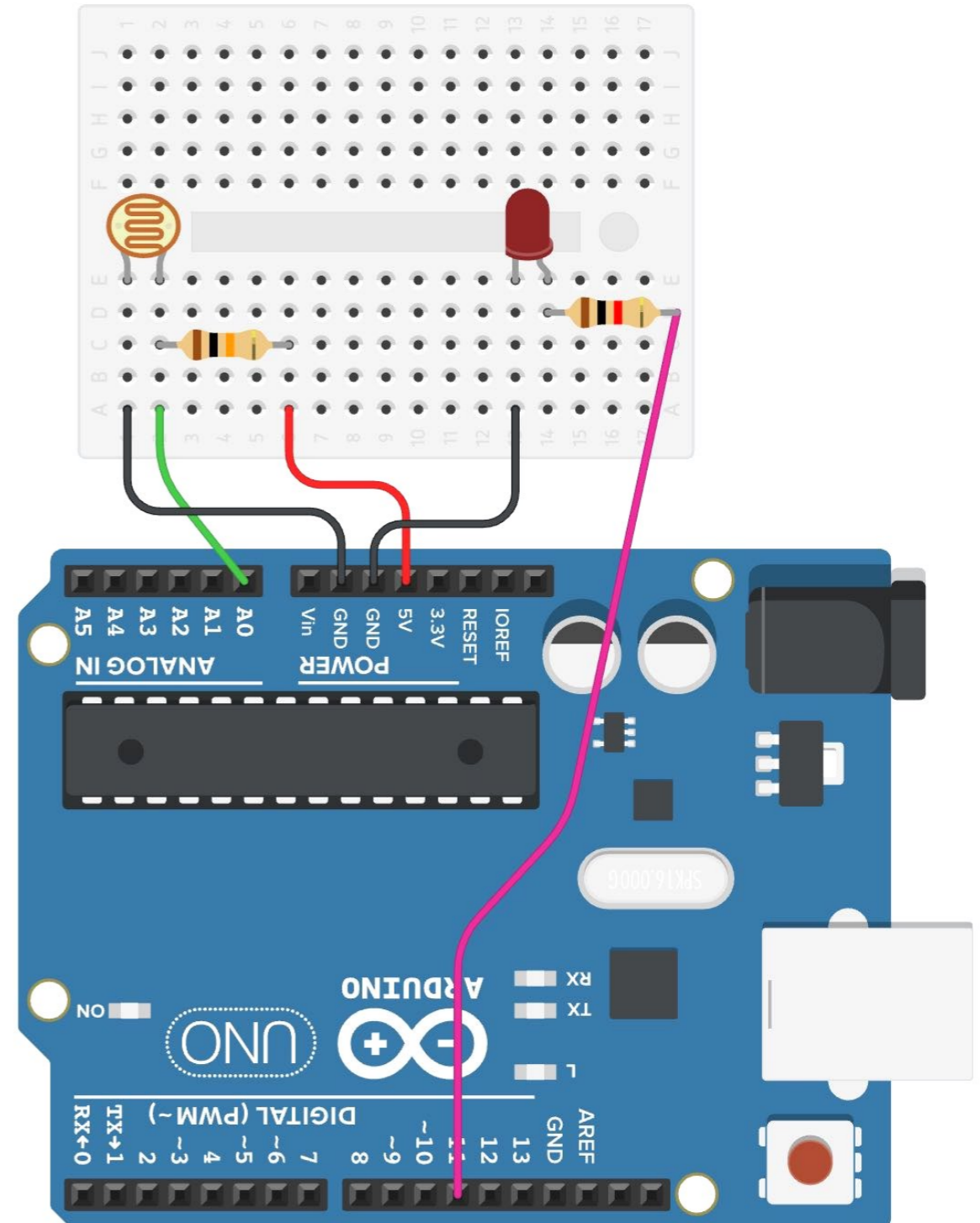
## Exercise PC1.2: Light Sensor

Build a circuit and code it to turn on an LED when it gets dark using a Photoresistor.

Optional: code it so the LED fades smoothly between dark and light states.




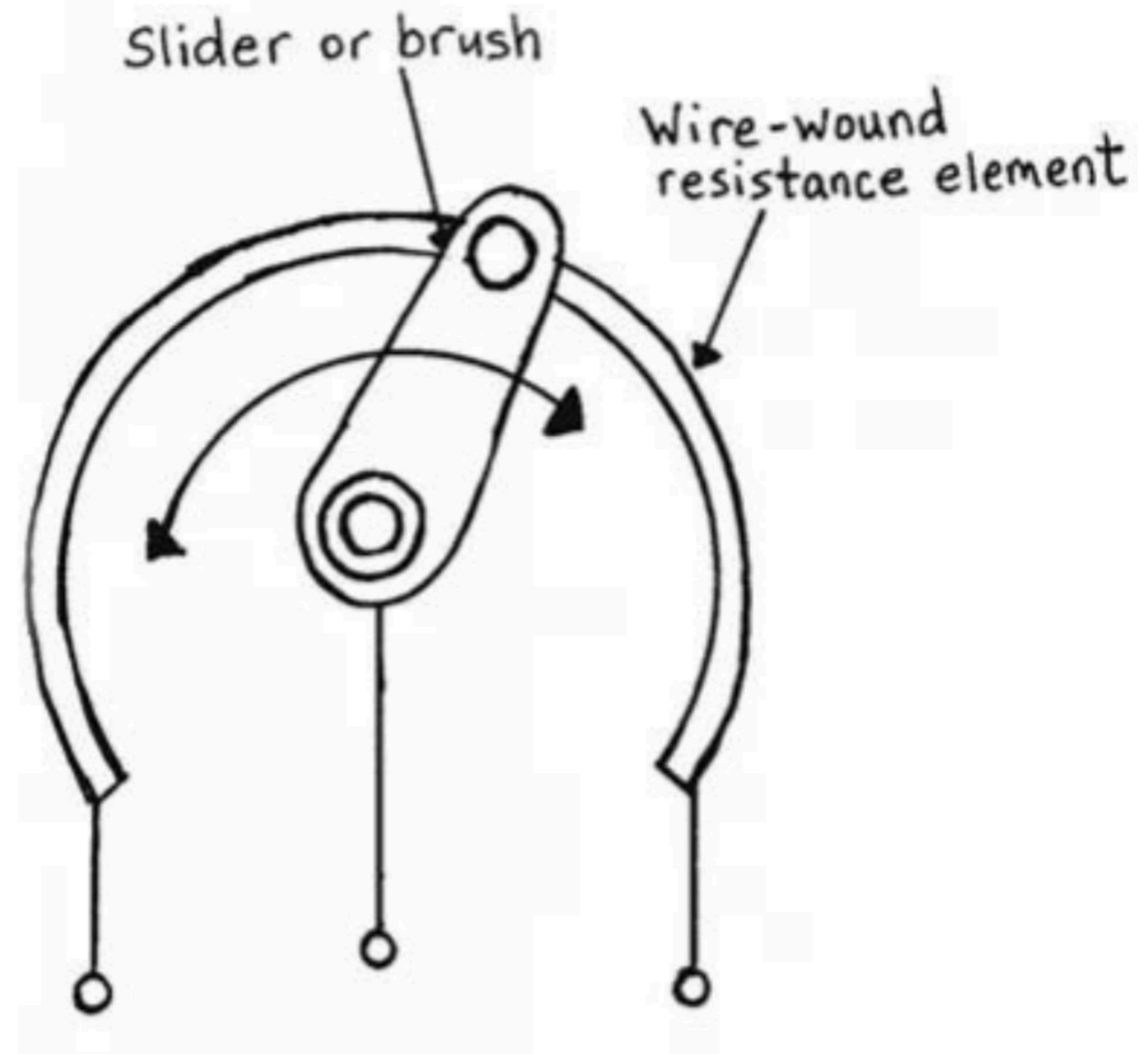A Potentiometer  
is also a voltage  
divider!





Potentiometer

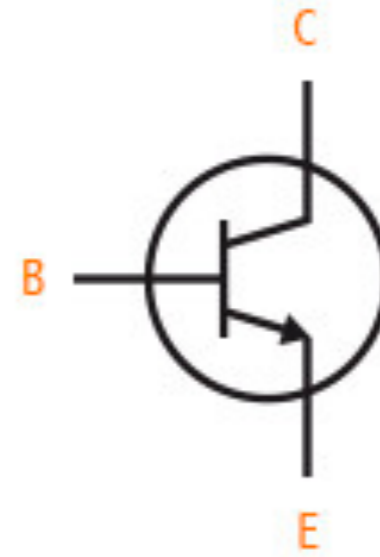
To power loads greater than the 40mA our Arduino digital pins can provide, we need to use a transistor.


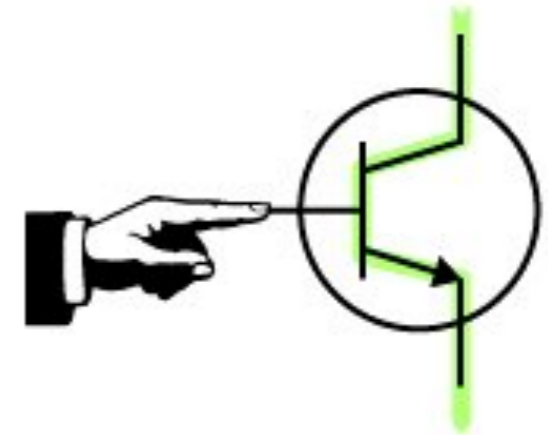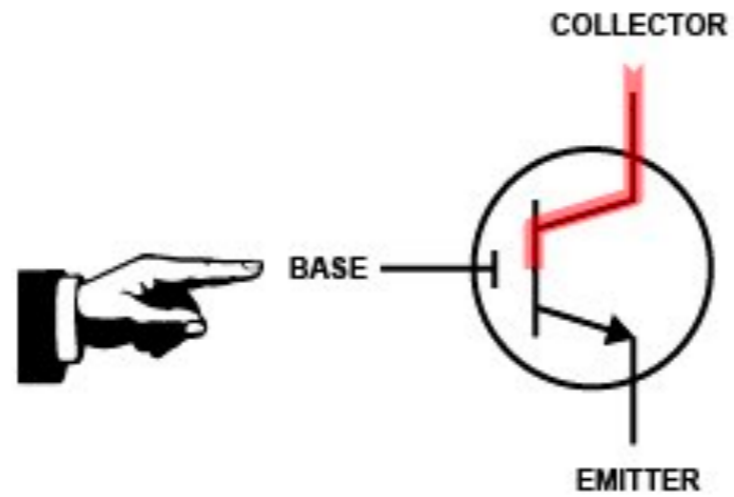
## Transistors

Transistors work like buttons, with a very small current on the base pin, allowing a larger current to flow between collector and emitter.



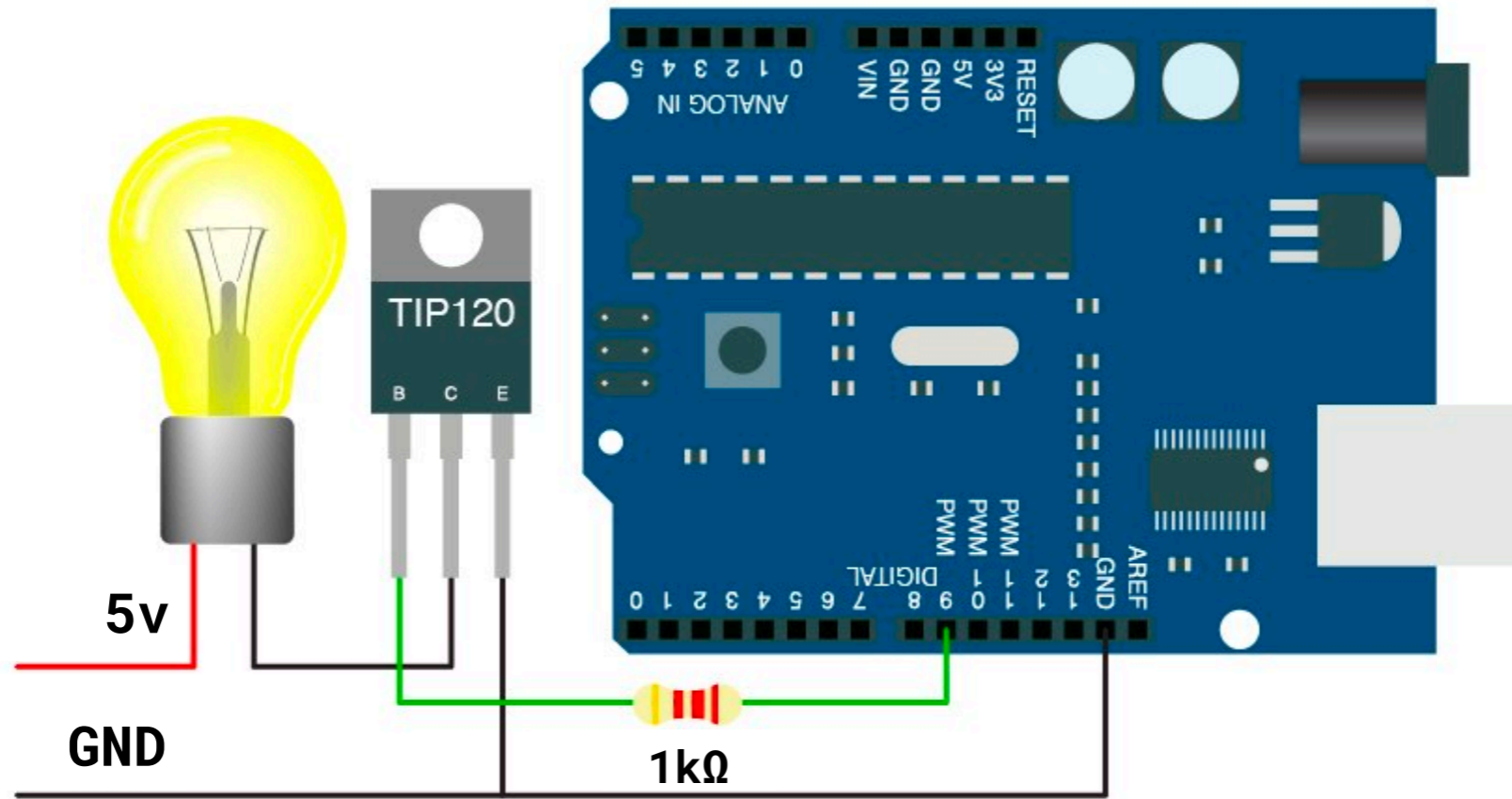


## Exercise PC1.3: Transistor with Lightbulb

Control an incandescent lightbulb using a transistor.

Can you also use PWM to dim it?




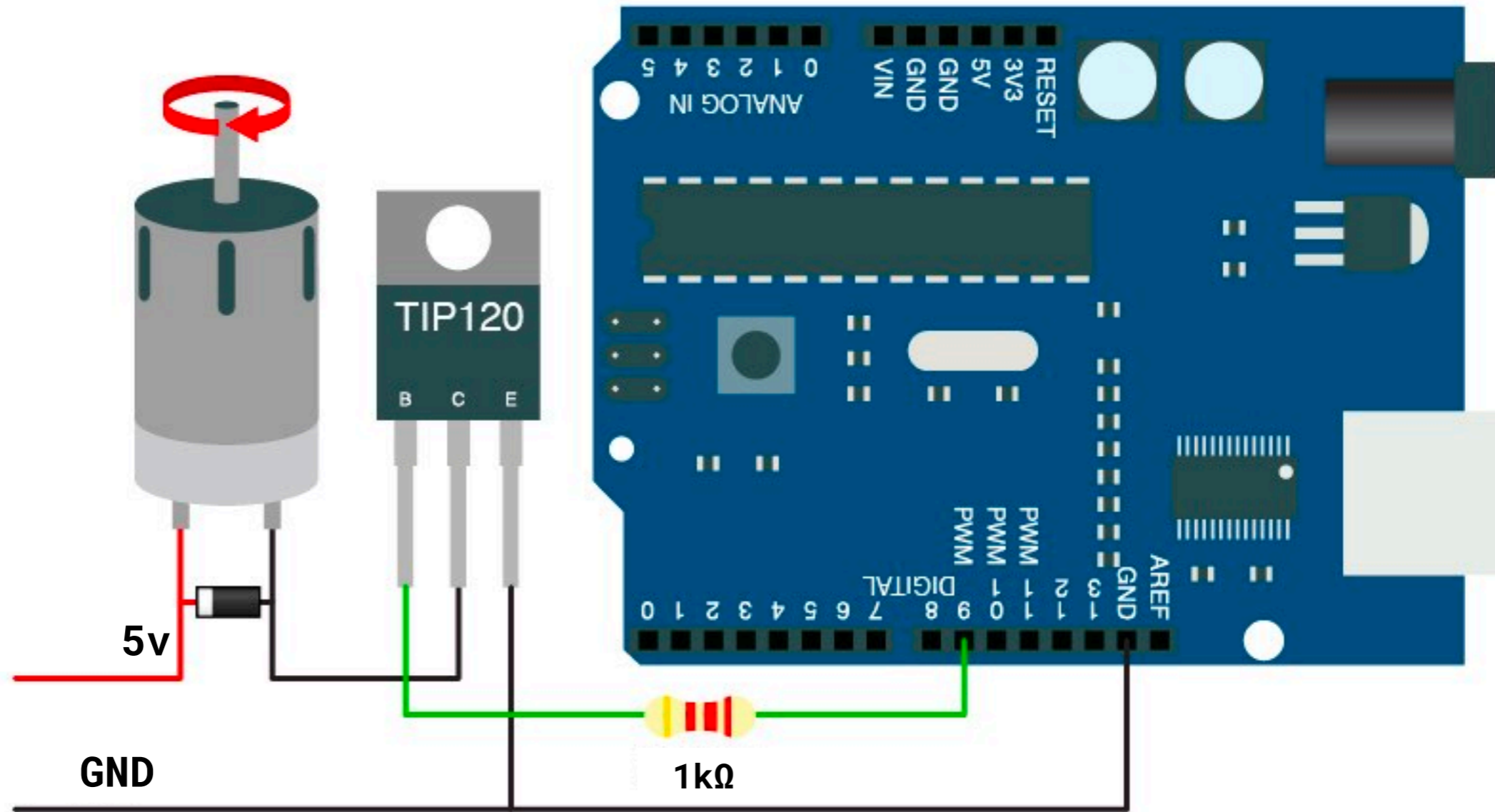Adding diode is important for inductive loads (motors for example)


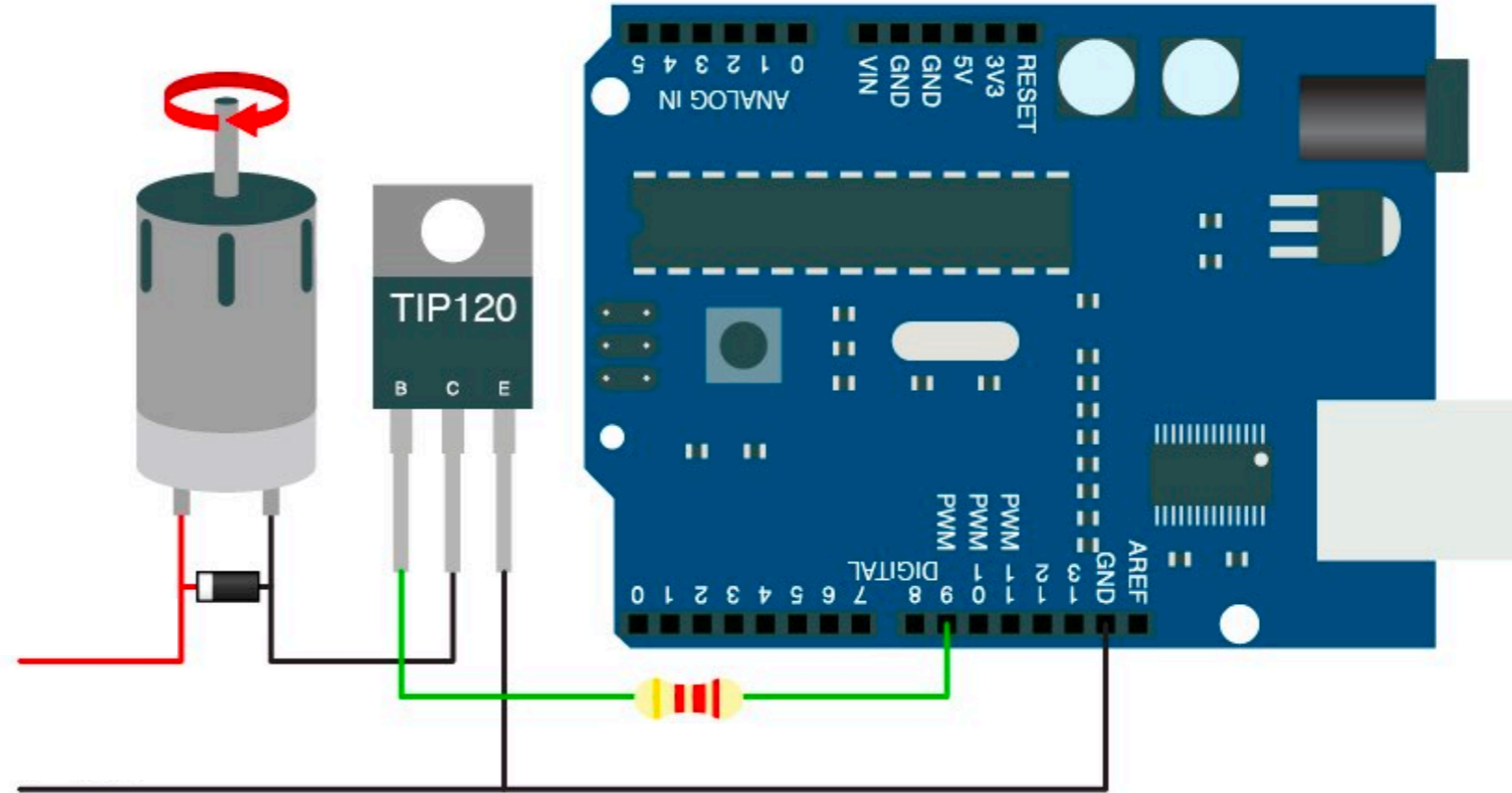
# Transistors


Adding diode is important for inductive loads!



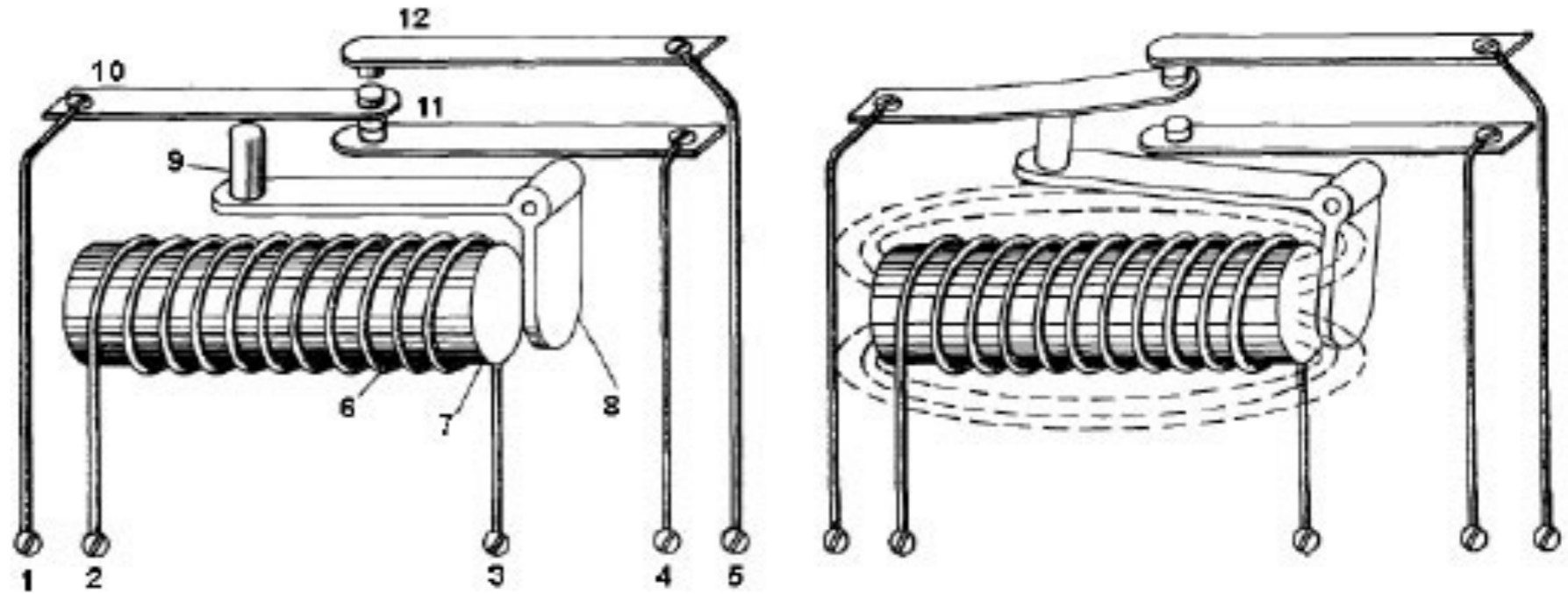
## Exercise PC1.4: Transistor with Motor

Hook up a motor in place of your lightbulb. Add in a potentiometer and write new code to control the motor speed by rotating a potentiometer.


Relays can sometimes be used instead of transistors (for controlling very high loads, or when the HV circuits need to be completely isolated). But, they are loud and slow!



## Relays

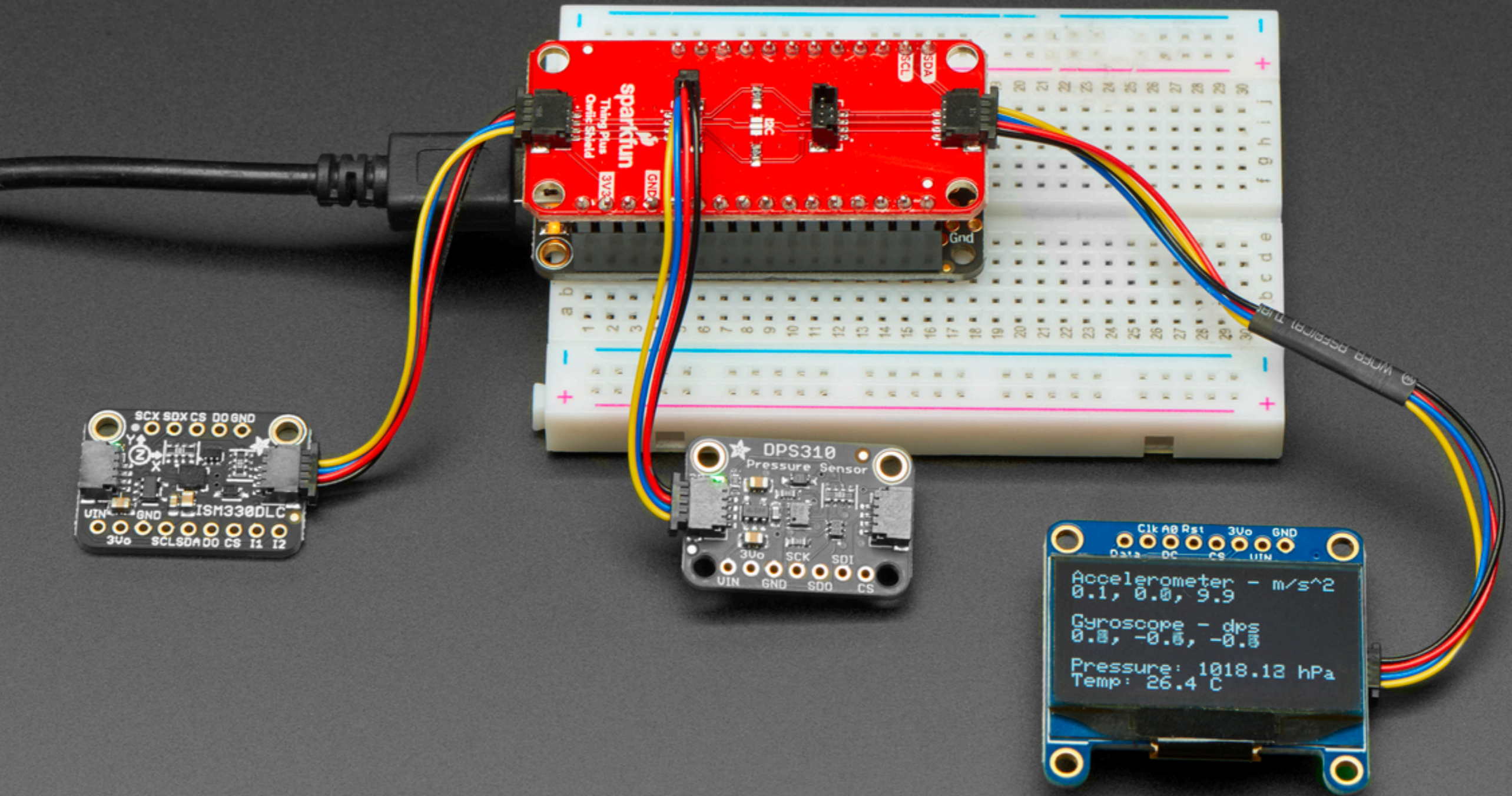

# Digital Peripherals and Protocols

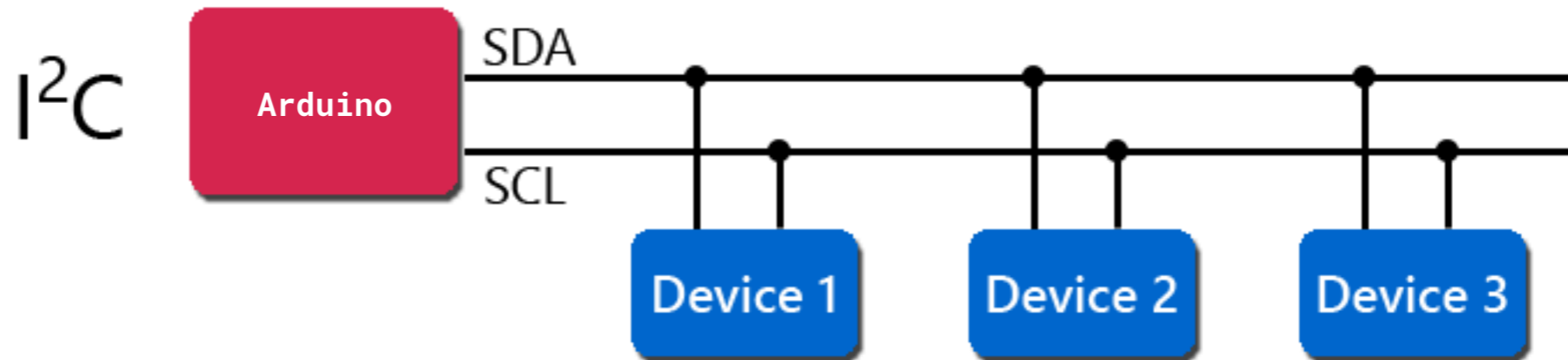


#### Uses:

- Communicating between Arduino and other chips (sensors or displays for example)
- Communicating between several Arduino boards on a small network


#### Limitations:

- Fairly slow (probably doesn't matter for our projects)
- I<sup>2</sup>C only works over short distances

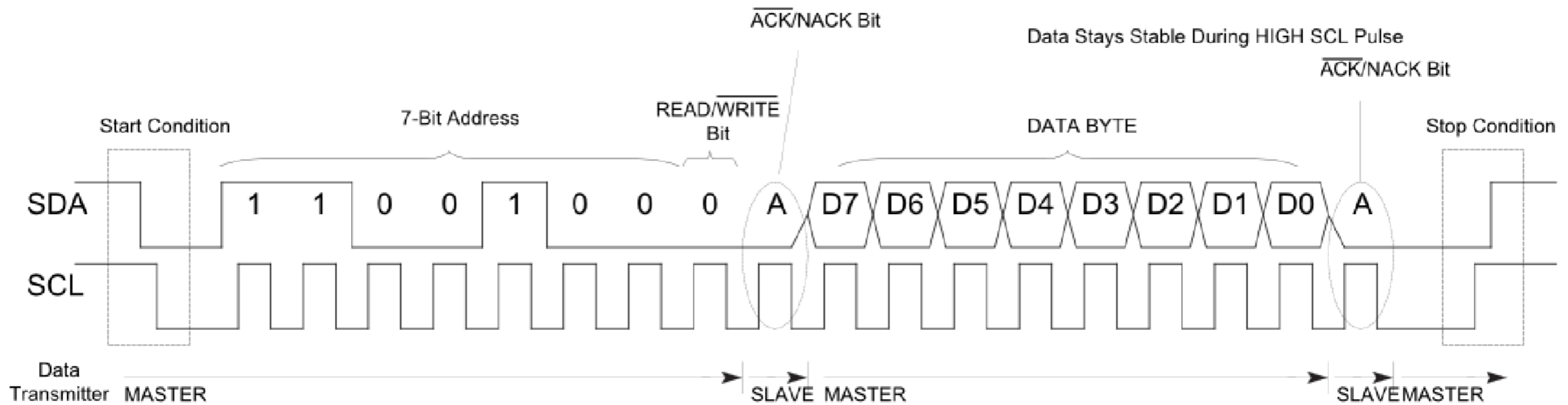
**I<sup>2</sup>C (Inter Integrated Circuit)**



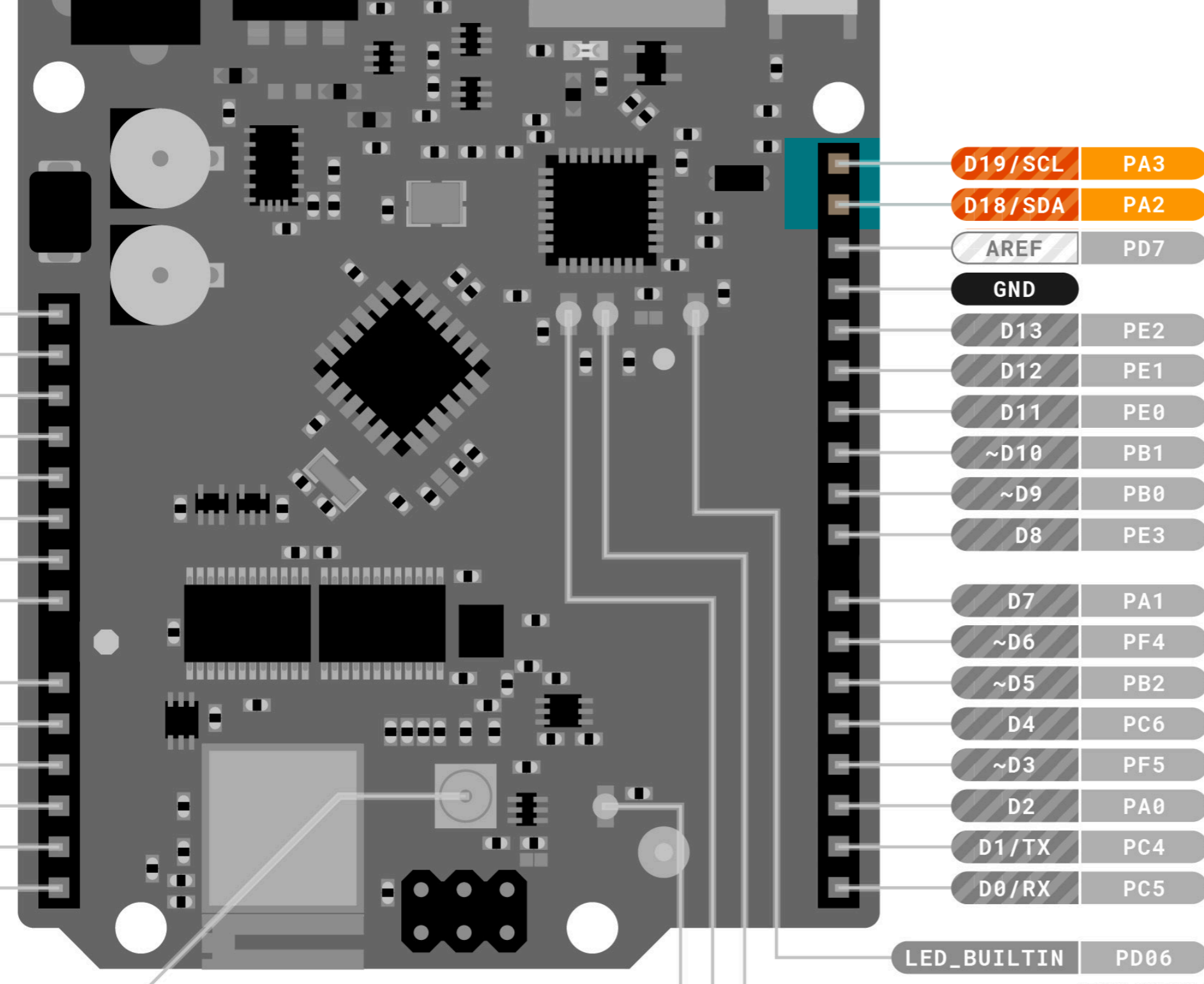**I<sup>2</sup>C (Inter Integrated Circuit)**



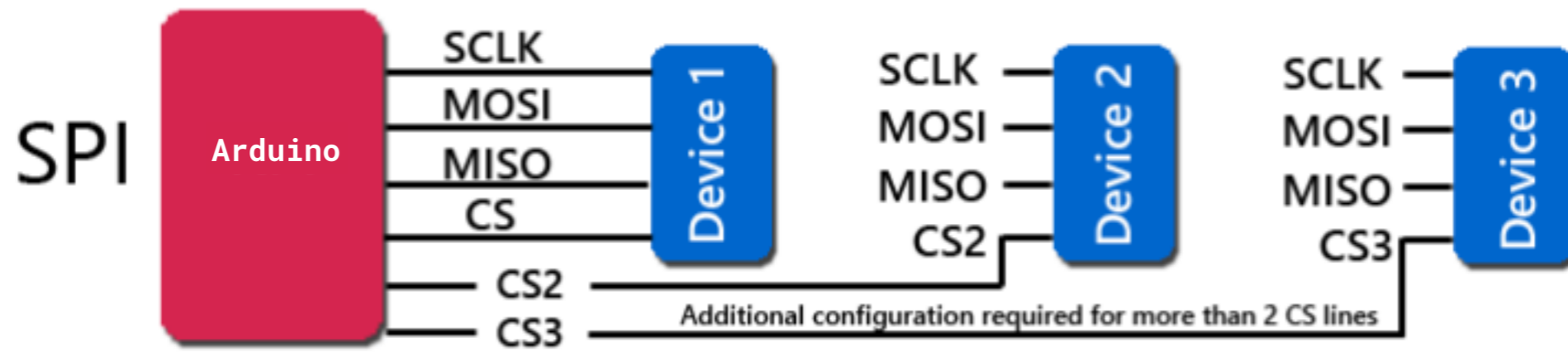**I<sup>2</sup>C (Inter Integrated Circuit)**



**Pros:**


- Faster than I<sup>2</sup>C

**Cons:**


- Needs more pins than I<sup>2</sup>C

**SPI (Serial Peripheral Interface)**




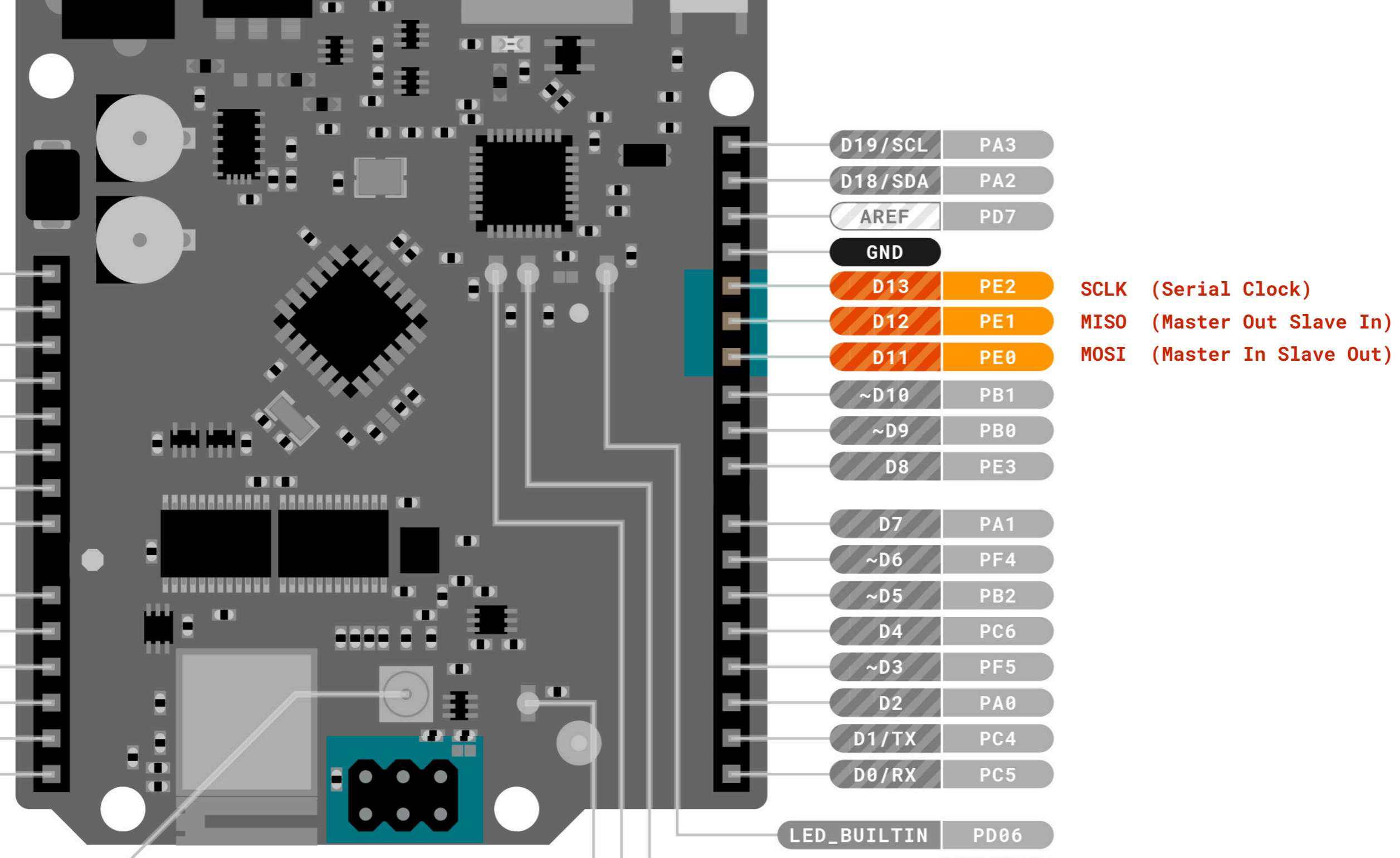


**SPI (Serial Peripheral Interface)**

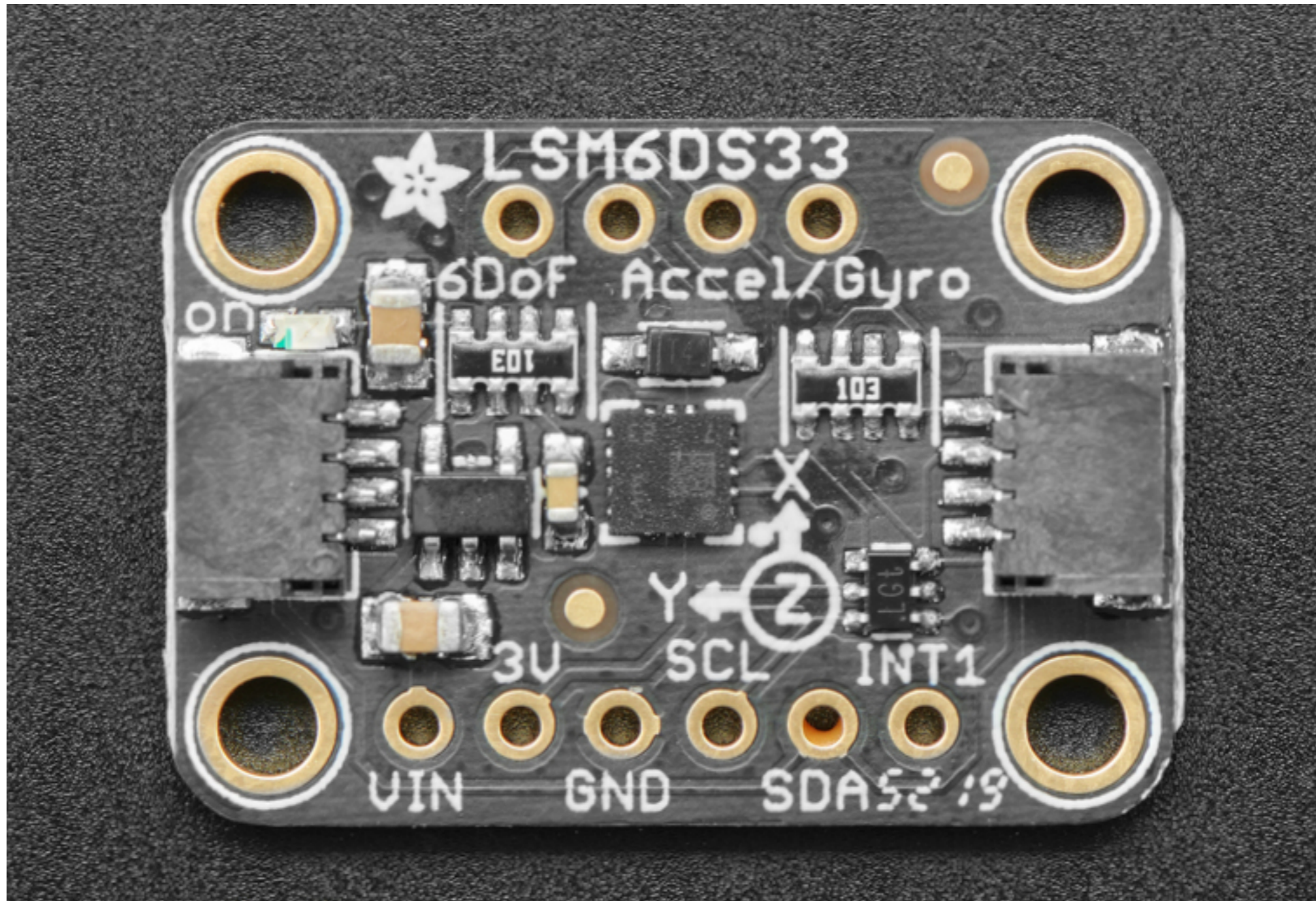

**Digital Peripherals**

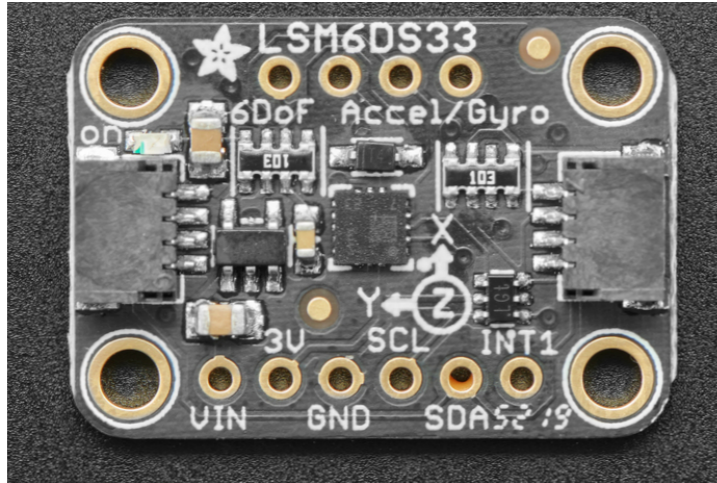


**LSM6DS33  
IMU**


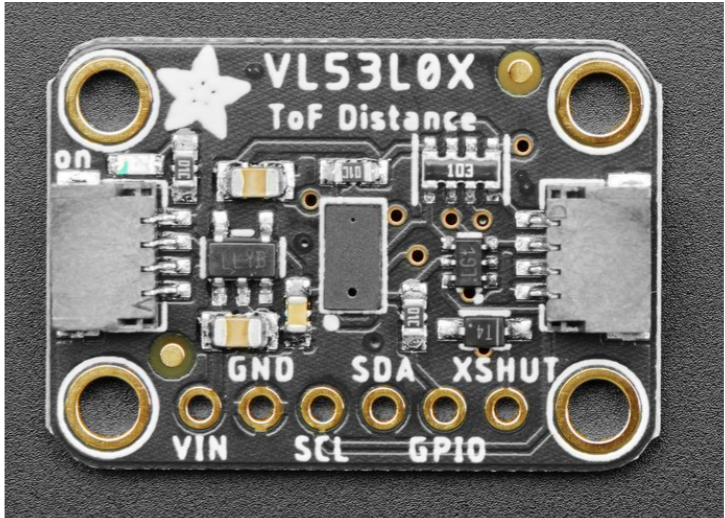


**VL53L0X  
Distance Sensor**



GYROSCOPE SENSING  
ANGULAR ORIENTATION

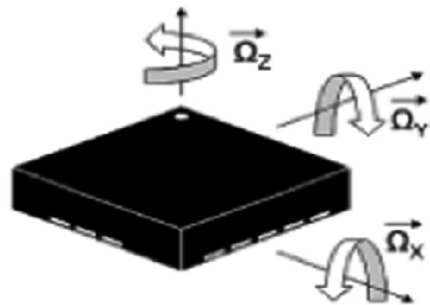

ACCELEROMETER SENSING  
AXIS ORIENTATION

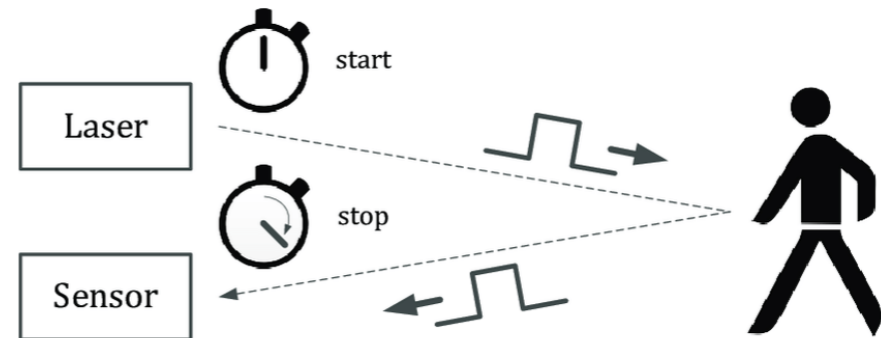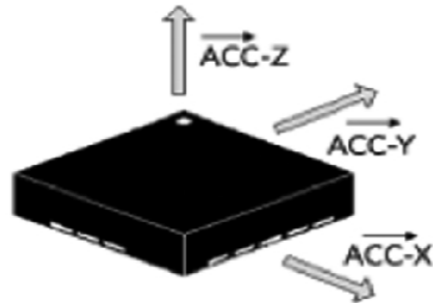


**Digital Sensors**

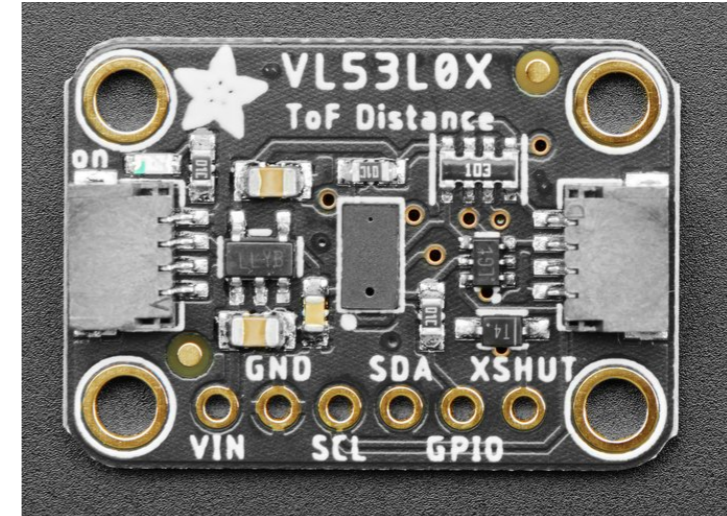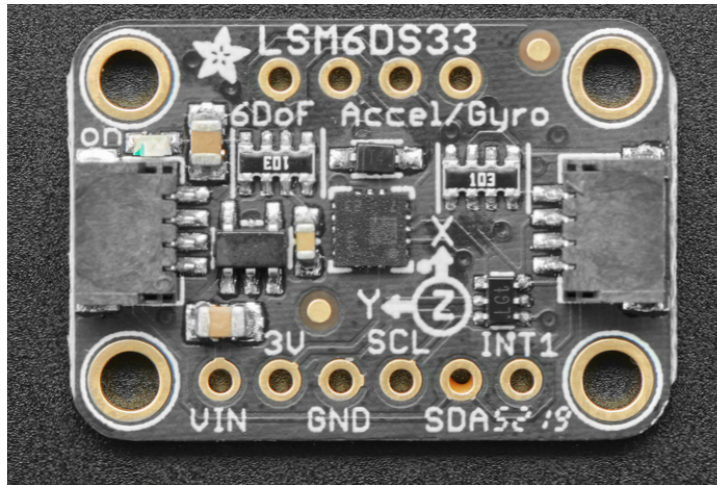

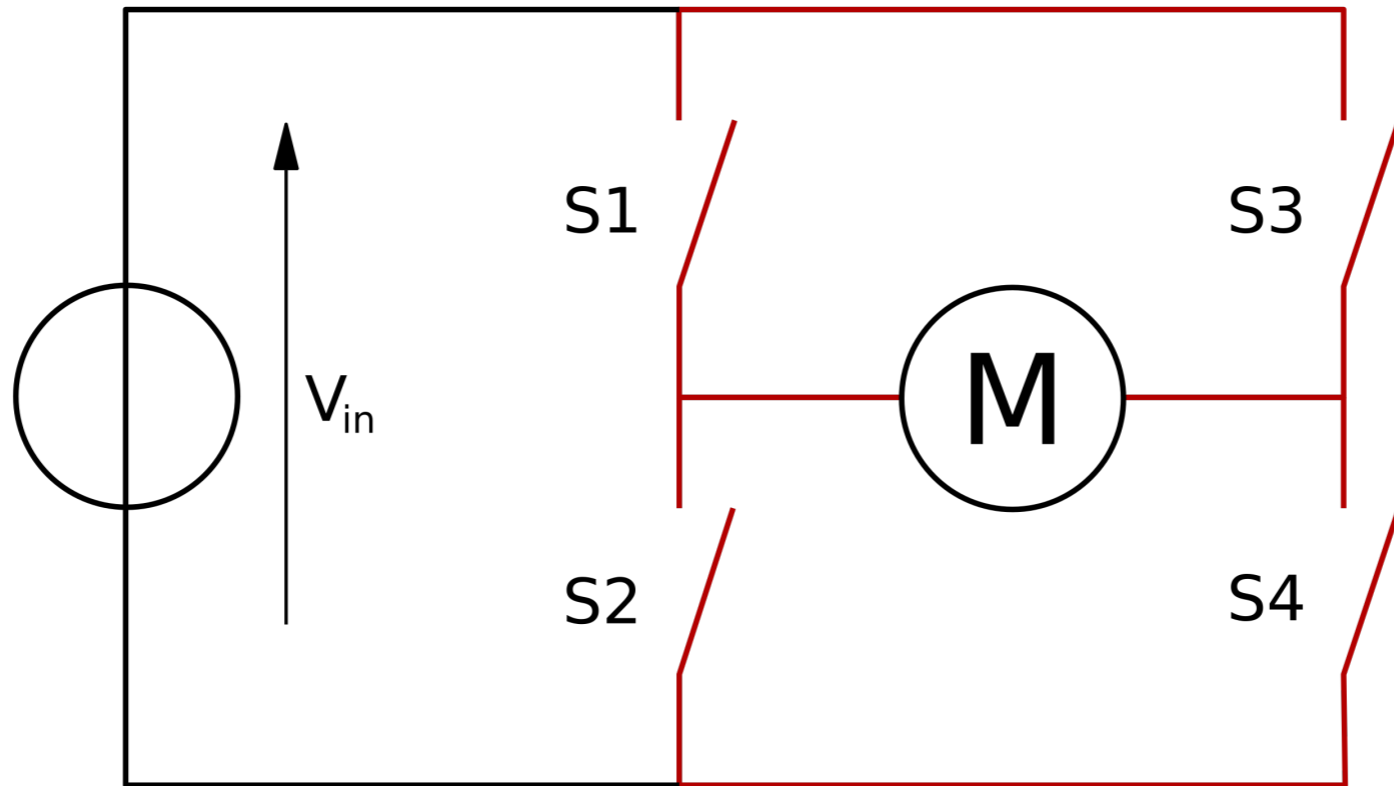
## Exercise PC2.0: Peripherals


Follow the hook up guide provided by Adafruit for your device. Use the data from your sensor to control one or more outputs, such as LEDs, motors or lightbulbs.




**H - Bridge**

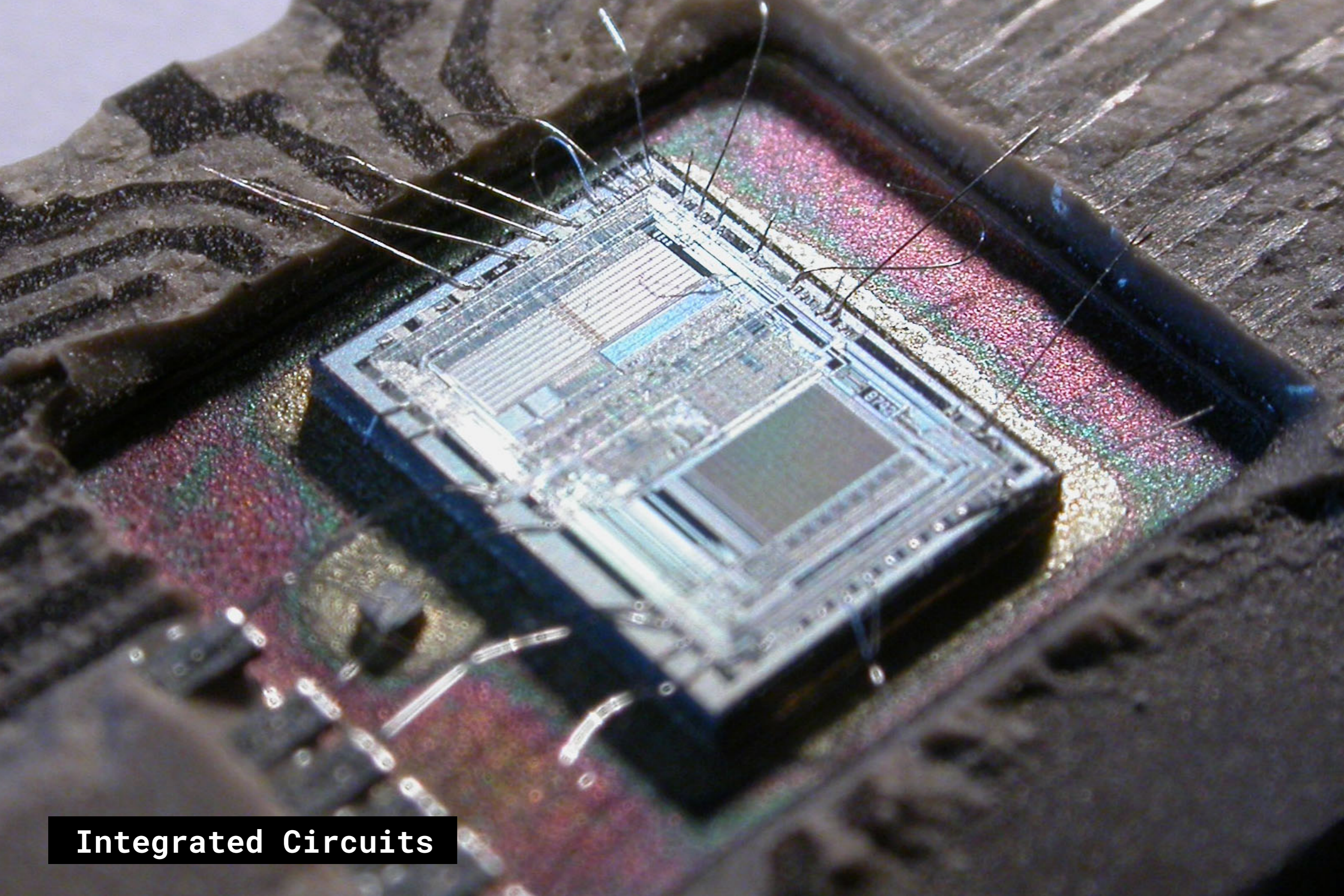

**Integrated Circuits**

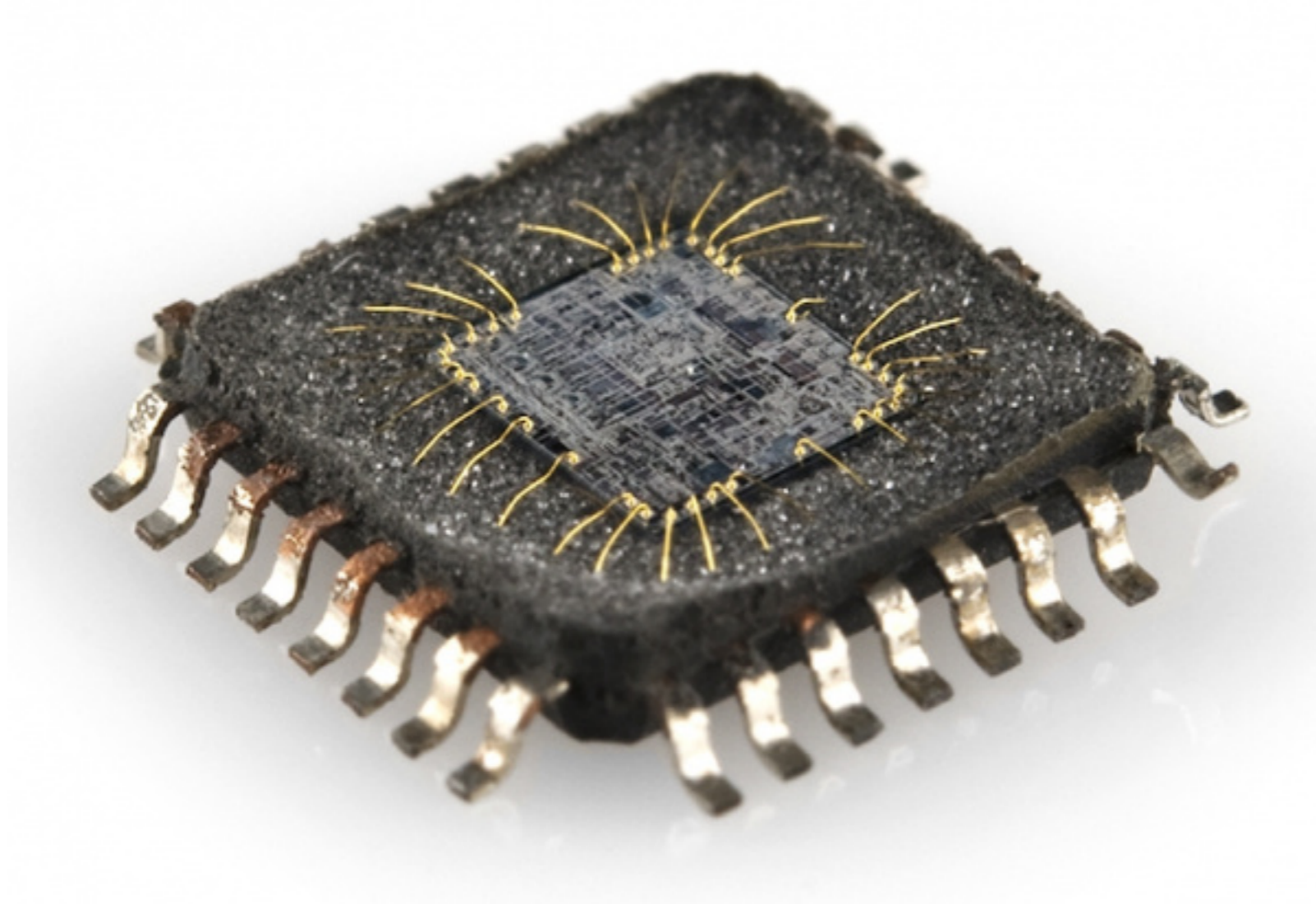

**Integrated Circuits**

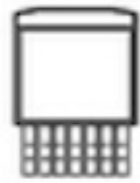

DDPAK




DPAK




DIP



SQP

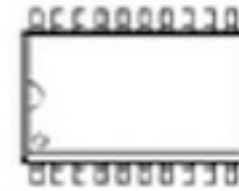

SW

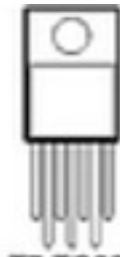

T7-TO220



FDIP



PDIP



PENTAWATT



TO220



TO2205



TO220ISO



PLCC



QDIP



QFP




TO252



TO263



TO268

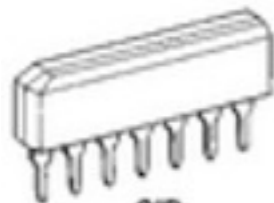

SIP



SO




SO8



TO3



TO52

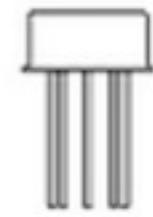

TO99



SOT223



SOT23



SQL




TSOP




ZIP

# Packages





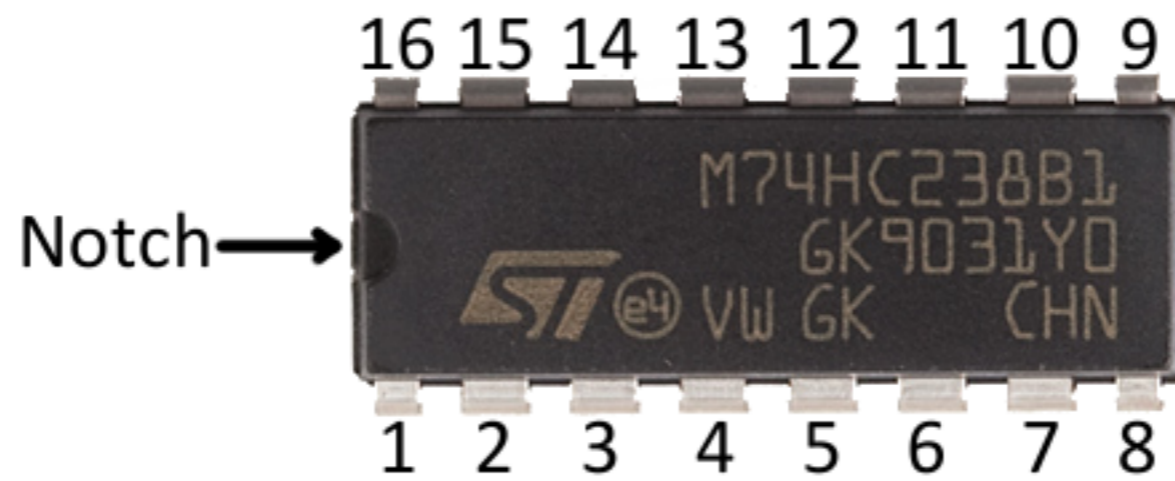


**Packages**

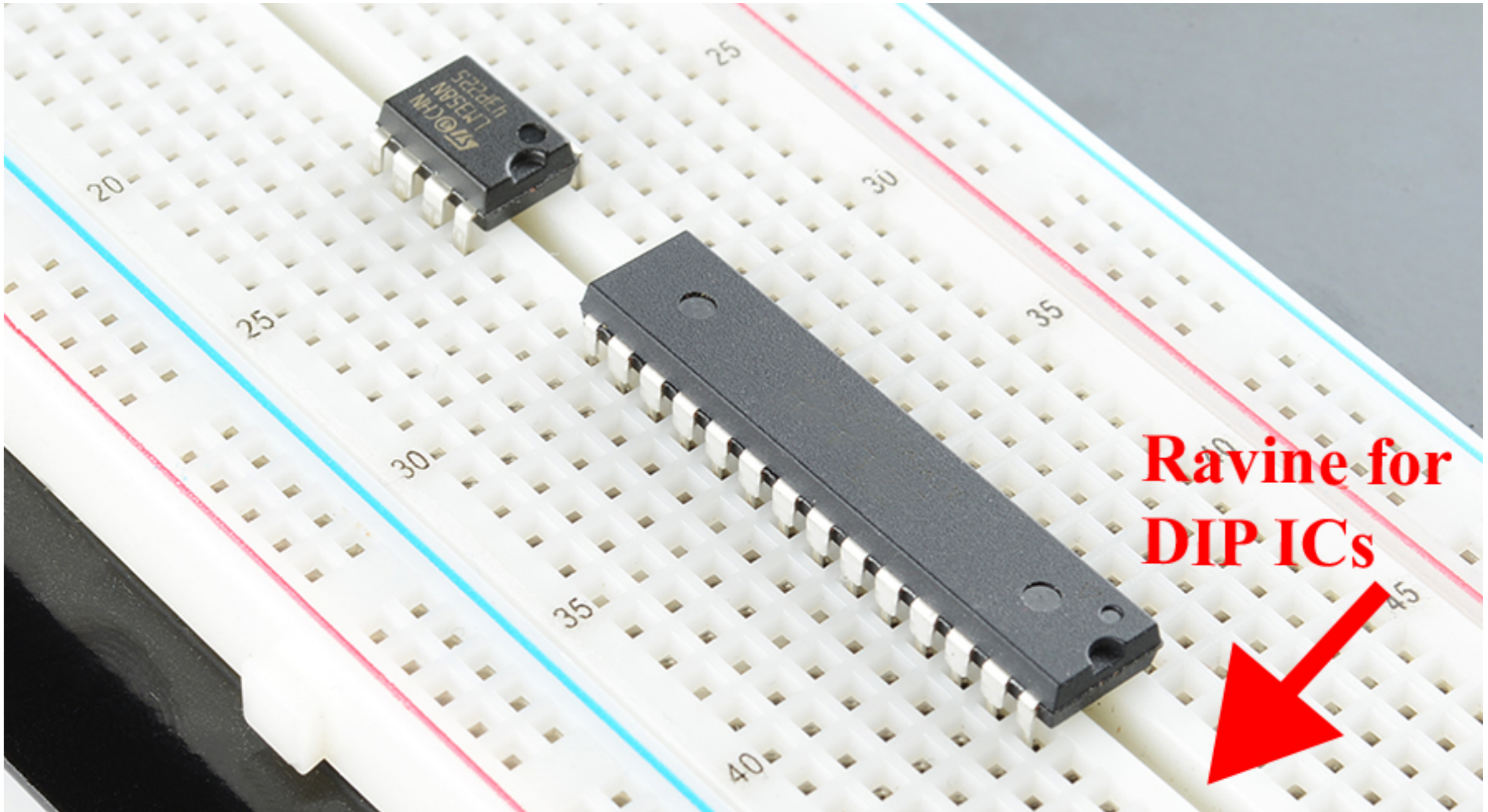


**Packages**

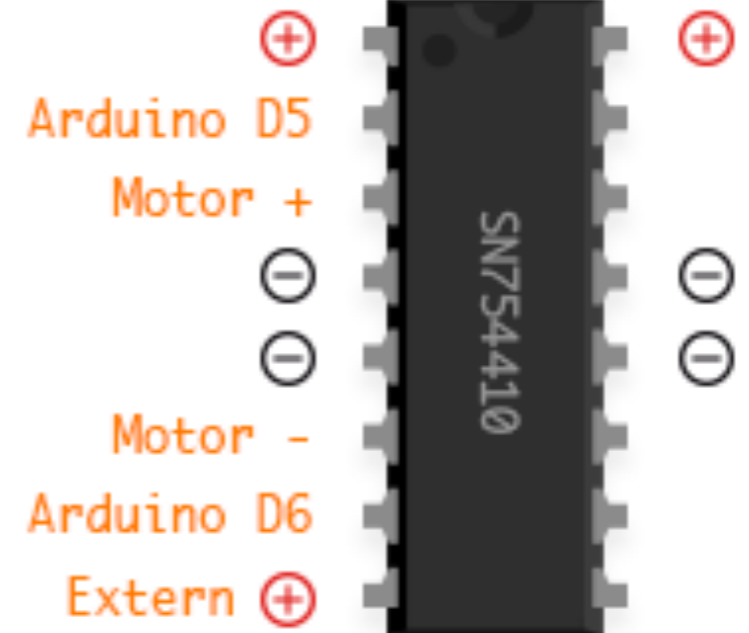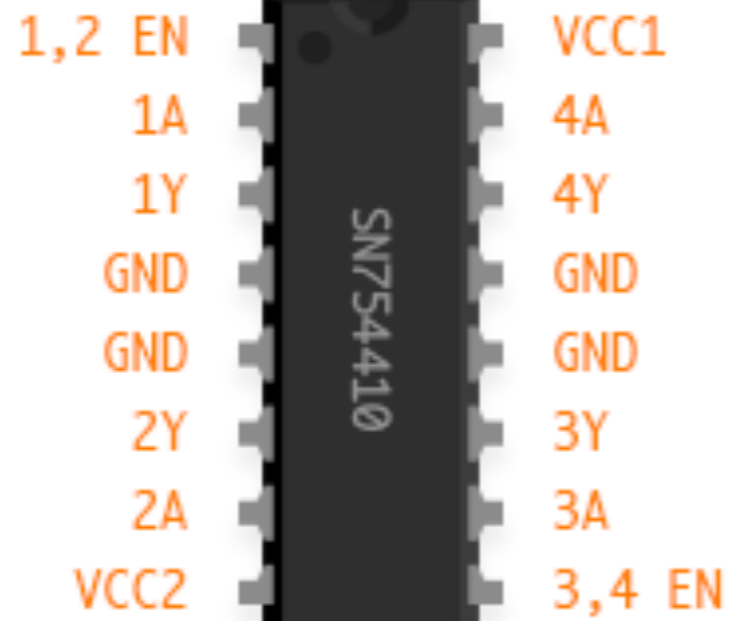


**H Bridge - SN754410**

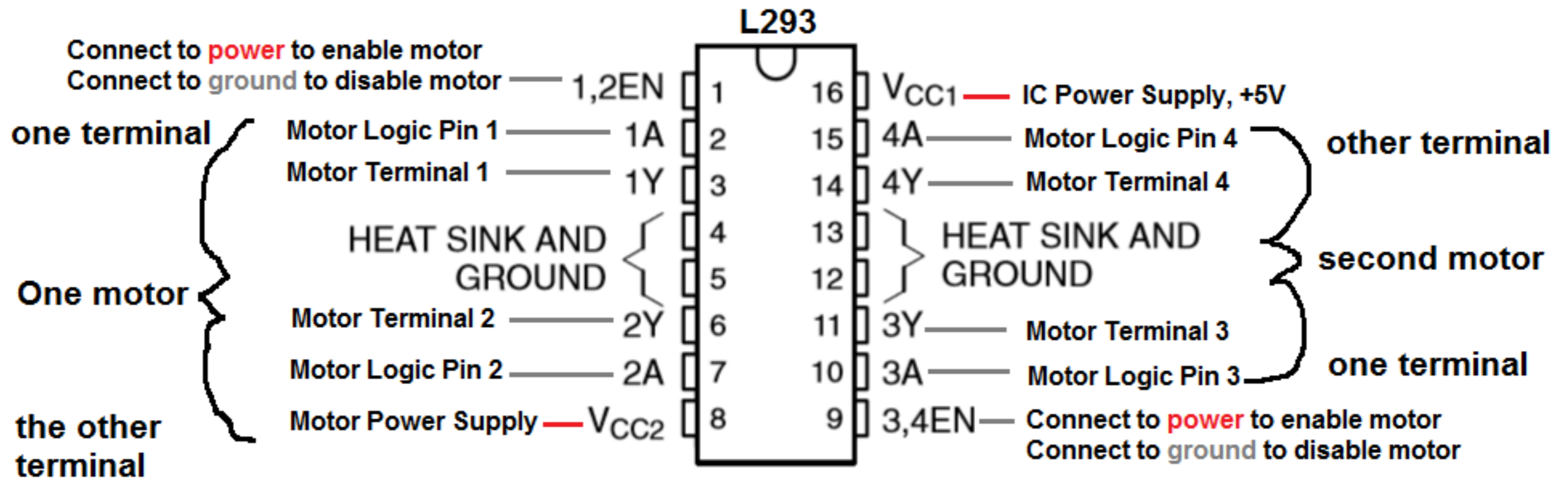

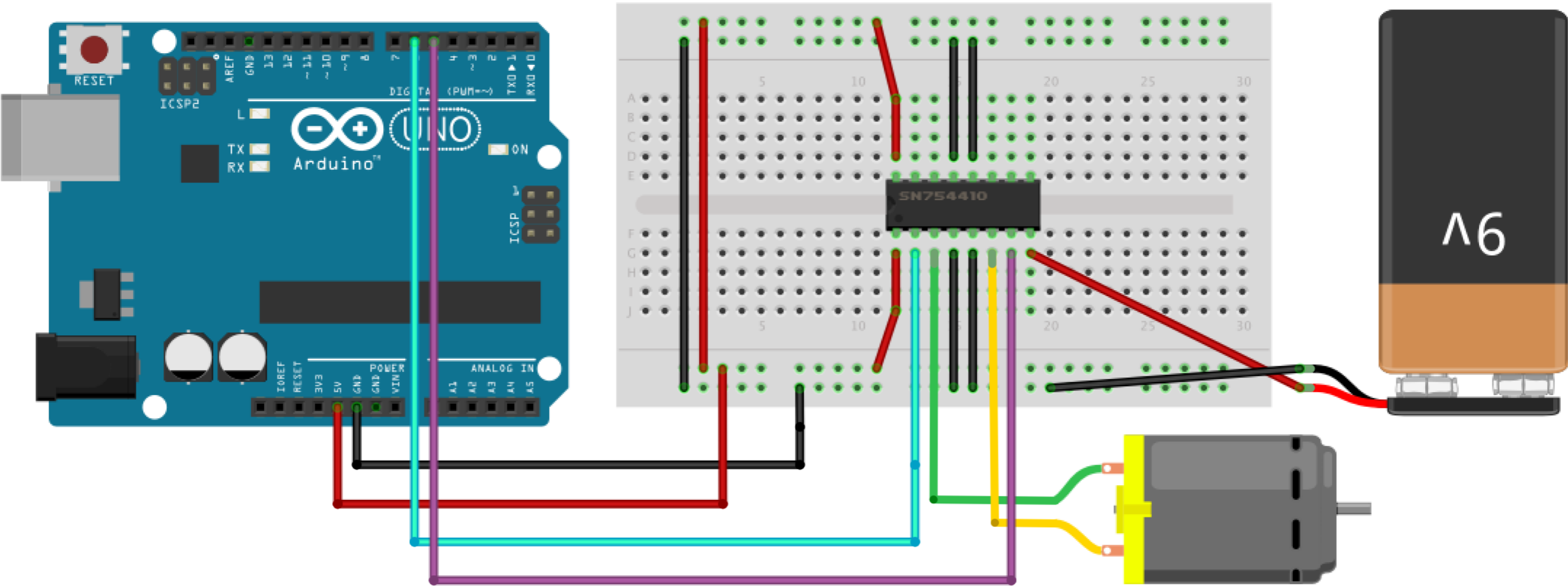

**SN754410 - hook-up**

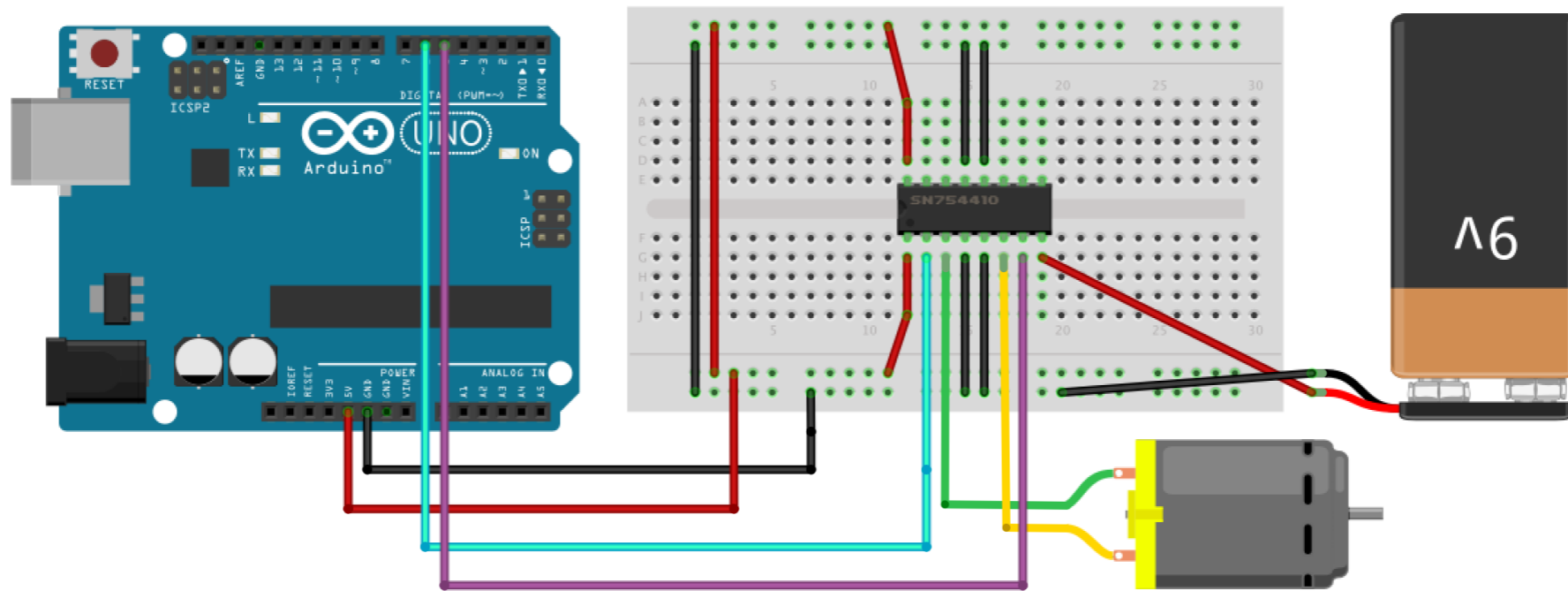

## Exercise PC3.0: H-Bridge

1. Use a push button to change the running direction of the motor using a h-bridge.
2. Add a way of controlling the speed too, such as a potentiometer.
3. Add an additional motor to your h-bridge